

The background features abstract, colorful swirls in shades of green, purple, and blue, interspersed with small yellow triangles, creating a dynamic and artistic feel.

# **Circuit Theory**

## **Chapter 9**

### **Sinusoidal Steady-State Analysis**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Sinusoids and Phasor

## Chapter 9

9.1 Motivation

9.2 Sinusoids' features

9.3 Phasors

9.4 Phasor relationships for circuit elements


9.5 Impedance and admittance

9.6 Kirchhoff's laws in the frequency domain


9.7 Impedance combinations

# 9.1 Motivation (1)

How to determine  $v(t)$  and  $i(t)$ ?

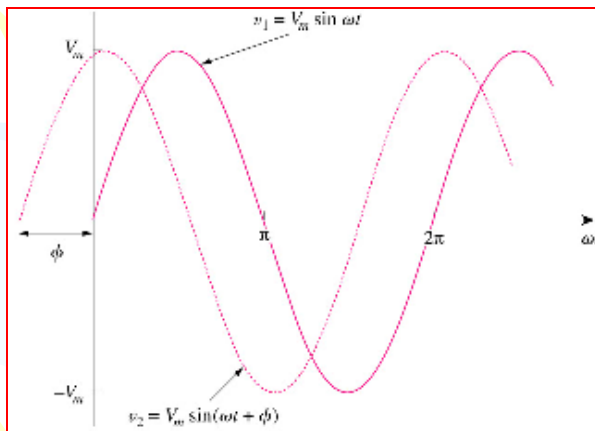

$$v_s(t) = 10V$$

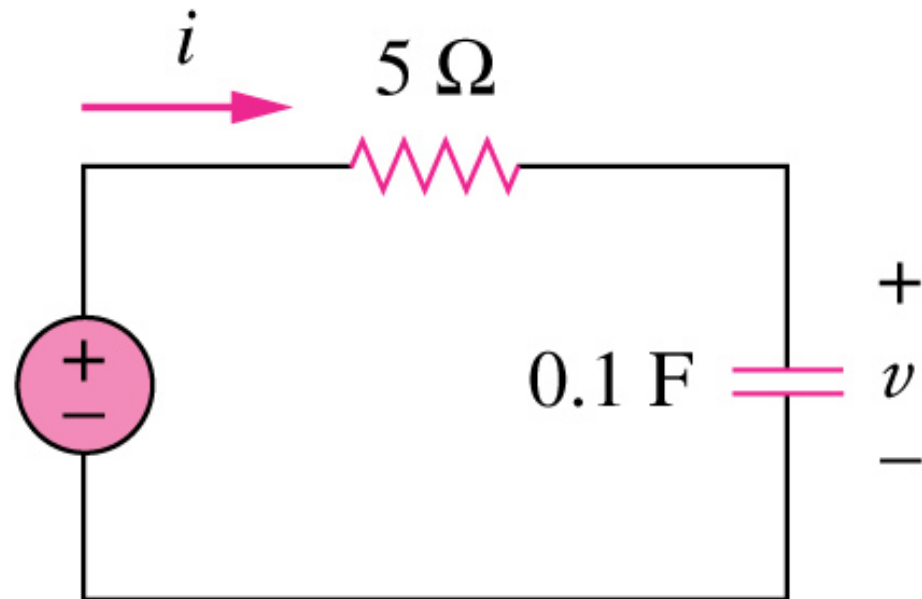


How can we apply what we have learned before to determine  $i(t)$  and  $v(t)$ ?


## 9.2 Sinusoids (1)

- A sinusoid is a signal that has the form of the sine or cosine function.
- A general expression for the sinusoid,

$$v(t) = V_m \sin(\omega t + \varphi)$$

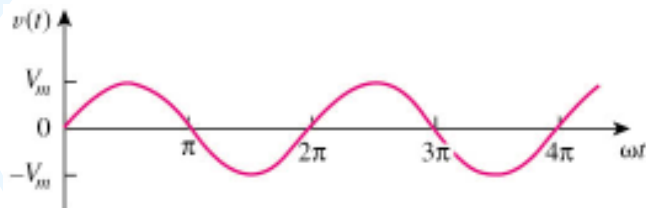

(a)

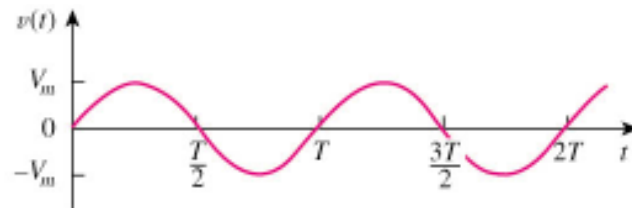

(b)

where


$V_m$  = the **amplitude** of the sinusoid

$\omega$  = the angular frequency in radians/s

$\Phi$  = the phase
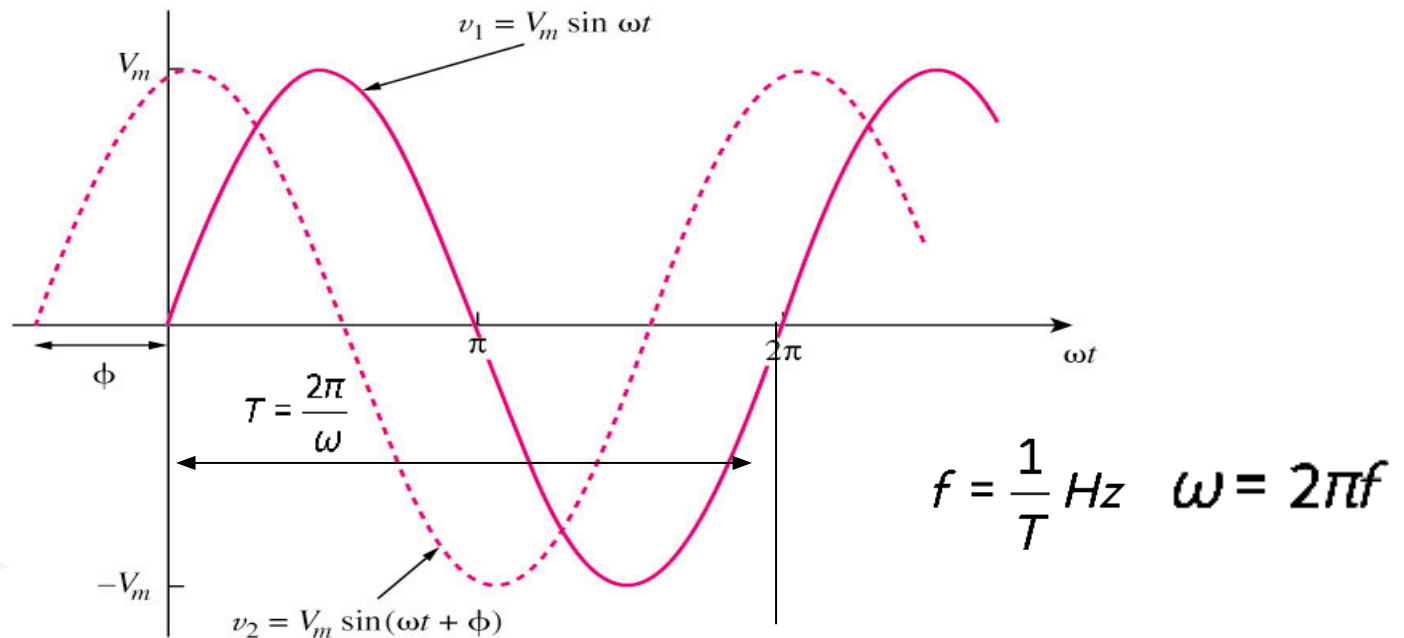
## 9.2 Sinusoids (2)

A **periodic function** is one that satisfies  $v(t) = v(t + nT)$ , for all  $t$  and for all integers  $n$ .



- Only two sinusoidal values with the **same frequency** can be compared by their amplitude and phase difference.
- If phase difference is zero, they are in phase; if phase difference is not zero, they are out of phase.



## 9.2 Sinusoids (3)

### **Example 1**

Given a sinusoid,  $5\sin(4\pi t - 60^\circ)$ , calculate its amplitude, phase, angular frequency, period, and frequency.

### **Solution:**

Amplitude = 5, phase =  $-60^\circ$ , angular frequency =  $4\pi$  rad/s, Period = 0.5 s, frequency = 2 Hz.

## 9.2 Sinusoids (4)

### Example 2

Find the phase angle between  $i_1 = -4\sin(377t + 25^\circ)$  and  $i_2 = 5\cos(377t - 40^\circ)$ , does  $i_1$  lead or lag  $i_2$ ?

### Solution:

Since  $\sin(\omega t + 90^\circ) = \cos \omega t$

$$i_2 = 5\sin(377t - 40^\circ + 90^\circ) = 5\sin(377t + 50^\circ)$$

$$i_1 = -4\sin(377t + 25^\circ) = 4\sin(377t + 180^\circ + 25^\circ) = 4\sin(377t + 205^\circ)$$

therefore,  $i_1$  leads  $i_2$   $155^\circ$ .


## 9.3 Phasor (1)

- A phasor is a complex number that represents the amplitude and phase of a sinusoid.
- It can be represented in one of the following three forms:

a. Rectangular  $z = x + jy = r(\cos \varphi + j \sin \varphi)$

b. Polar  $z = r \angle \varphi$

c. Exponential  $z = re^{j\varphi}$

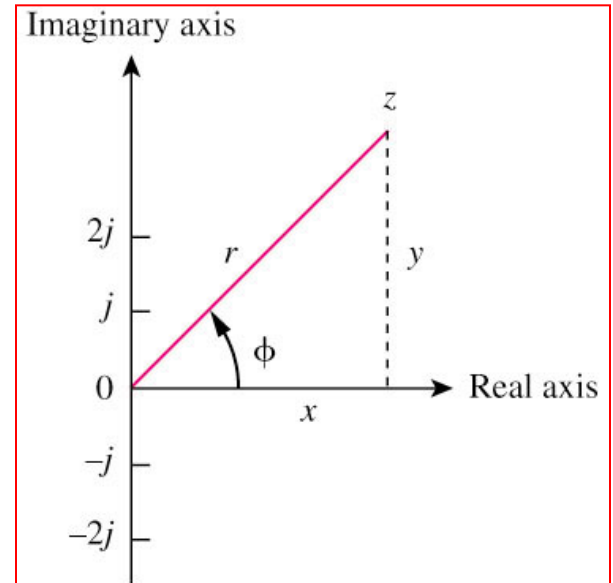

where

$$r = \sqrt{x^2 + y^2}$$

$$\varphi = \tan^{-1} \frac{y}{x}$$





## 9.3 Phasor (2)

### Example 3

- Evaluate the following complex numbers:

a.  $[(5 + j2)(-1 + j4) - 5 \angle 60^\circ]$

b.  $\frac{10 + j5 + 3 \angle 40^\circ}{-3 + j4} + 10 \angle 30^\circ$

### Solution:

a.  $-15.5 + j13.67$

b.  $8.293 + j2.2$

## 9.3 Phasor (3)

### Mathematic operation of complex number:

1. Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

2. Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

3. Multiplication

$$z_1 z_2 = r_1 r_2 \angle \varphi_1 + \varphi_2$$

4. Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \varphi_1 - \varphi_2$$

5. Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle -\varphi$$

6. Square root

$$\sqrt{z} = \sqrt{r} \angle \varphi/2$$

7. Complex conjugate

$$z^* = x - jy = r \angle -\varphi = re^{-j\varphi}$$

8. Euler's identity

$$e^{\pm j\varphi} = \cos \varphi \pm j \sin \varphi$$

## 9.3 Phasor (4)

- Transform a sinusoid to and from the time domain to the phasor domain:

$$v(t) = V_m \cos(\omega t + \varphi) \longleftrightarrow V = V_m \angle \varphi$$

(time domain)

(phasor domain)

- Amplitude and phase difference are two principal concerns in the study of voltage and current sinusoids.
- Phasor will be defined from the cosine function in all our proceeding study. If a voltage or current expression is in the form of a sine, it will be changed to a cosine by subtracting from the phase.

## 9.3 Phasor (5)

### Example 4

Transform the following sinusoids to phasors:

$$i = 6\cos(50t - 40^\circ) \text{ A}$$

$$v = -4\sin(30t + 50^\circ) \text{ V}$$

### Solution:

a.  $I = 6\angle -40^\circ \text{ A}$

b. Since  $-\sin(A) = \cos(A+90^\circ)$ ;

$$v(t) = 4\cos(30t+50^\circ+90^\circ) = 4\cos(30t+140^\circ) \text{ V}$$

Transform to phasor  $\Rightarrow V = 4\angle 140^\circ \text{ V}$

## 9.3 Phasor (6)

### Example 5:

Transform the following phasors to sinusoids:

a.  $\mathbf{V} = -10\angle 30^\circ \text{ V}$

b.  $\mathbf{I} = j(5 - j12) \text{ A}$

### Solution:

a)  $v(t) = 10\cos(\omega t + 210^\circ) \text{ V}$

b) Since  $\mathbf{I} = 12 + j5 = \sqrt{12^2 + 5^2} \angle \tan^{-1}(\frac{5}{12}) = 13\angle 22.62^\circ$   
 $i(t) = 13\cos(\omega t + 22.62^\circ) \text{ A}$



## 9.3 Phasor (7)

### The differences between $v(t)$ and $V$ :

- $v(t)$  is instantaneous or time-domain representation  
 $V$  is the frequency or phasor-domain representation.
- $v(t)$  is time dependent,  $V$  is not.
- $v(t)$  is always real with no complex term,  $V$  is generally complex.

Note: Phasor analysis applies only when frequency is constant; when it is applied to two or more sinusoid signals only if they have the same frequency.

## 9.3 Phasor (8)

Relationship between differential, integral operation in phasor listed as follow:

$$v(t) \longleftrightarrow V = V \angle \varphi$$

$$\frac{dv}{dt} \longleftrightarrow j\omega V$$

$$\int v dt \longleftrightarrow \frac{V}{j\omega}$$

## 9.3 Phasor (9)

### Example 6

Use phasor approach, determine the current  $i(t)$  in a circuit described by the integro-differential equation.


$$4i + 8\int i dt - 3\frac{di}{dt} = 50\cos(2t + 75^\circ)$$

Answer:  $i(t) = 4.642\cos(2t + 143.2^\circ) \text{ A}$


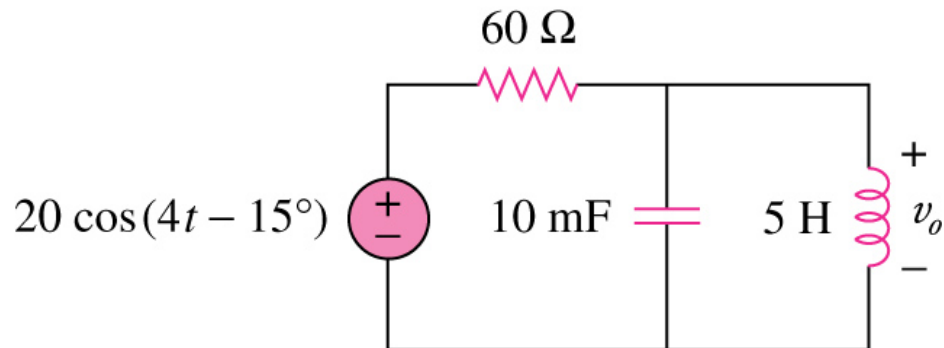
## 9.3 Phasor (10)

- In-class exercise for Unit 6a, we can derive the differential equations for the following circuit in order to solve for  $v_o(t)$  in phase domain  $V_o$ .



$$\frac{d^2 v_o}{dt^2} + \frac{5}{3} \frac{dv_o}{dt} + 20v_o = -\frac{400}{3} \sin(4t - 15^\circ)$$

- However, the derivation may sometimes be very tedious.

**Is there any quicker and more systematic methods to do it?**




## 9.3 Phasor (11)

**The answer is YES!**


Instead of first deriving the differential equation and then transforming it into phasor to solve for  $V_o$ , we can transform all the RLC components into phasor first, then apply the KCL laws and other theorems to set up a phasor equation involving  $V_o$  directly.

# 9.4 Phasor Relationships for Circuit Elements (1)


Resistor:

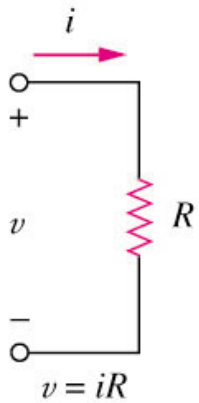


(a)

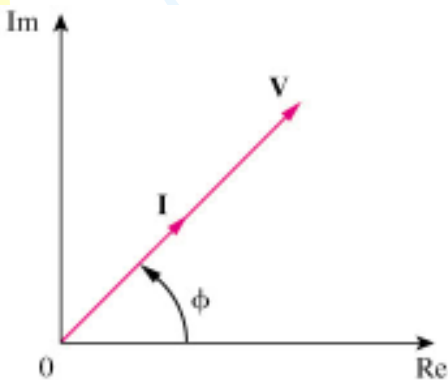

Inductor:

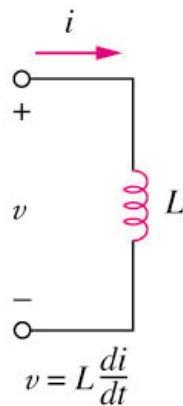


(a)

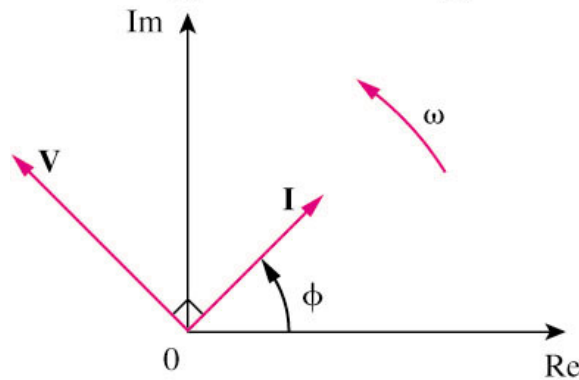


(b)

Capacitor:

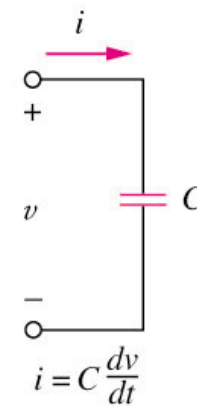

(a)

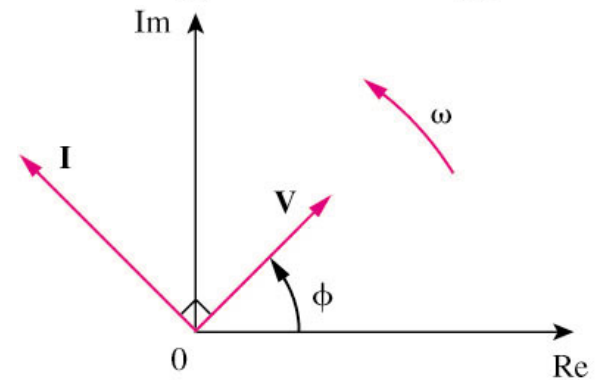

(b)

## 9.4 Phasor Relationships for Circuit Elements (2)

### Summary of voltage-current relationship

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

## 9.4 Phasor Relationships for Circuit Elements (3)

### Example 7

If voltage  $v(t) = 6\cos(100t - 30^\circ)$  is applied to a  $50\ \mu\text{F}$  capacitor, calculate the current,  $i(t)$ , through the capacitor.

Answer:  $i(t) = \underline{30\ \cos(100t + 60^\circ)\ \text{mA}}$

# 9.5 Impedance and Admittance (1)

- The impedance  $Z$  of a circuit is the ratio of the phasor voltage  $V$  to the phasor current  $I$ , measured in ohms  $\Omega$ .

$$Z = \frac{V}{I} = R + jX$$

where  $R = \text{Re}, Z$  is the resistance and  $X = \text{Im}, Z$  is the reactance. **Positive  $X$  is for  $L$  and negative  $X$  is for  $C$ .**

- The admittance  $Y$  is the reciprocal of impedance, measured in siemens (S).

$$Y = \frac{1}{Z} = \frac{I}{V}$$

## 9.5 Impedance and Admittance (2)

### Impedances and admittances of passive elements

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

# 9.5 Impedance and Admittance (3)




$$Z = j\omega L$$



Short circuit at dc


$$\omega = 0; Z = 0$$

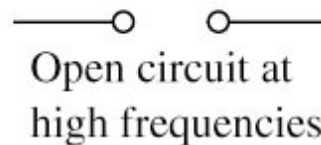


Open circuit at high frequencies

$$\omega \rightarrow \infty; Z \rightarrow \infty$$

(a)

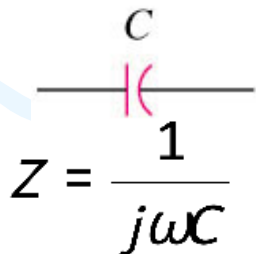


$$Z = \frac{1}{j\omega C}$$

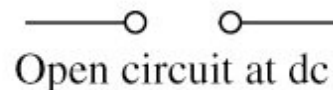

Open circuit at dc

$$\omega = 0; Z \rightarrow \infty$$

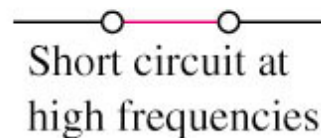

Short circuit at high frequencies

$$\omega \rightarrow \infty; Z = 0$$

(b)



## 9.5 Impedance and Admittance (4)


After we know how to convert RLC components from time to phasor domain, we can transform a time domain circuit into a phasor/frequency domain circuit.

Hence, we can apply the KCL laws and other theorems to directly set up phasor equations involving our target variable(s) for solving.

# 9.5 Impedance and Admittance (5)
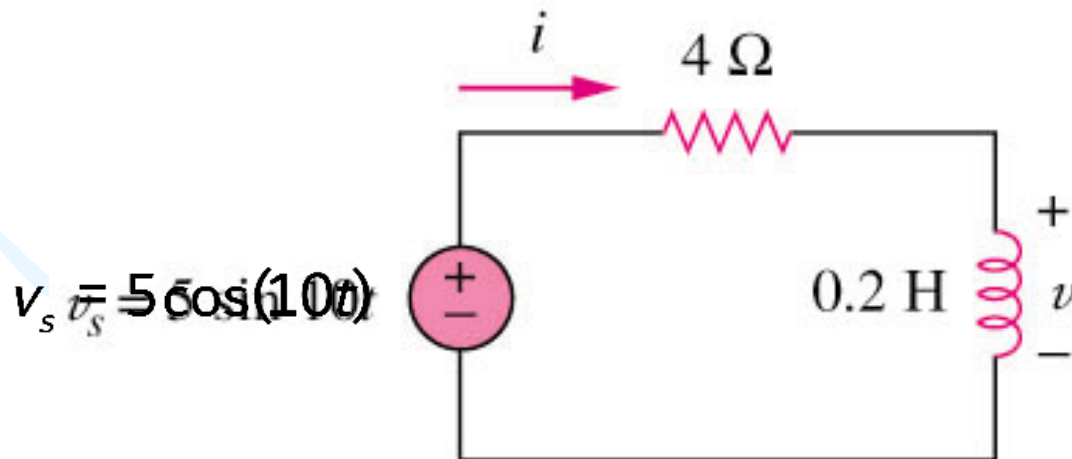
## Example 8

Refer to Figure below, determine  $v(t)$  and  $i(t)$ .



Answers:  $i(t) = 1.118 \cos(10t - 26.56^\circ) \text{ A}$ ;  $v(t) = 2.236 \cos(10t + 63.43^\circ) \text{ V}$



## 9.6 Kirchhoff's Laws in the Frequency Domain (1)

- Both KVL and KCL are hold in the phasor domain or more commonly called frequency domain.
- Moreover, the variables to be handled are phasors, which are complex numbers.
- All the mathematical operations involved are now in complex domain.

The background features a stylized sun in the top left corner, composed of a large yellow circle with several yellow triangular rays extending from it. Below the sun, there are three balloons: a light blue one, a light green one, and a light purple one, each with yellow triangular rays. The overall style is simple and colorful.


## 9.7 Impedance Combinations (1)

- The following principles used for DC circuit analysis all apply to AC circuit.
- For example:
  - a. voltage division
  - b. current division
  - c. circuit reduction
  - d. impedance equivalence
  - e. Y- $\Delta$  transformation

## 9.7 Impedance Combinations (2)
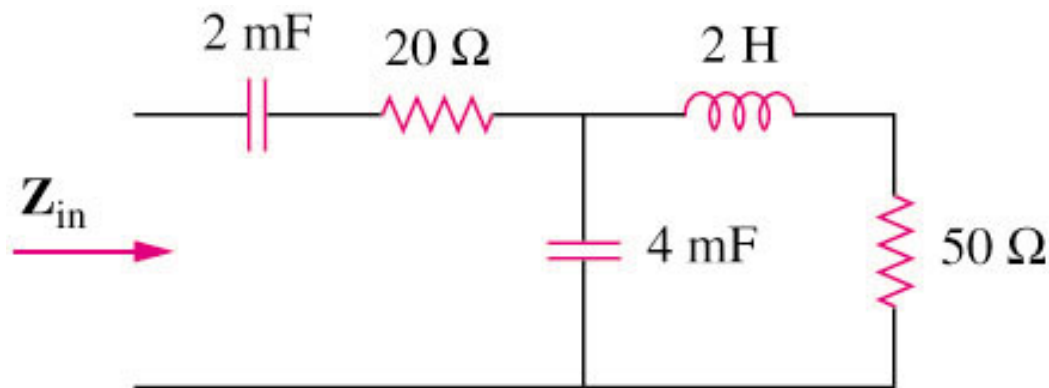
### Example 9

Determine the input impedance of the circuit in figure below at  $\omega = 10$  rad/s.



Answer:  $Z_{in} = 32.38 - j73.76$