

OP-AMP APPLICATIONS

CHAPTER II



Common Op-Amp Applications

Constant-gain amplifier

Voltage summing

Voltage buffer

Controlled sources


Instrumentation circuits

Active filters




Constant-Gain Amplifier

Inverting amplifier

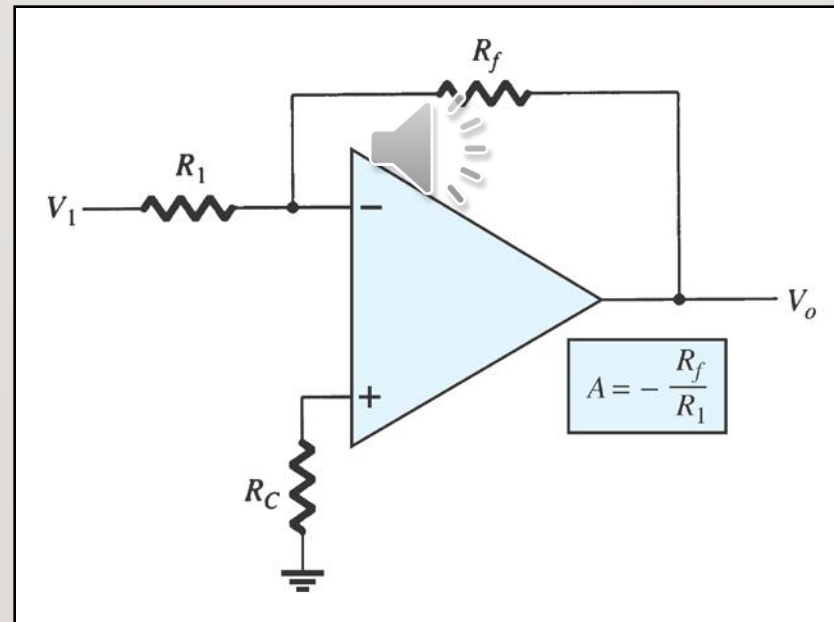

Constant-Gain inverting Amplifier

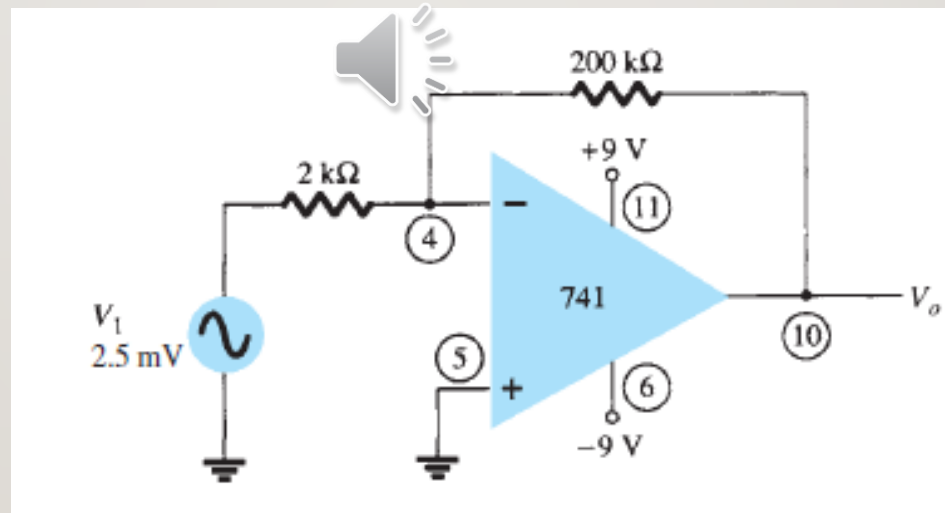Example 11.1: Determine the output voltage of a given circuit with a sinusoidal input voltage of 2.5mV



Constant-Gain inverting Amplifier

Example 11.1 Solution: It is clear from the circuit that it is a constant gain inverting amplifier so


$$A = -\frac{R_f}{R_1} = -\frac{200 \text{ k}\Omega}{2 \text{ k}\Omega} = -100$$

The output voltage is then

$$V_o = AV_i = -100(2.5 \text{ mV}) = -250 \text{ mV} = -0.25 \text{ V}$$


Constant-Gain Non inverting Amplifier

Noninverting amplifier

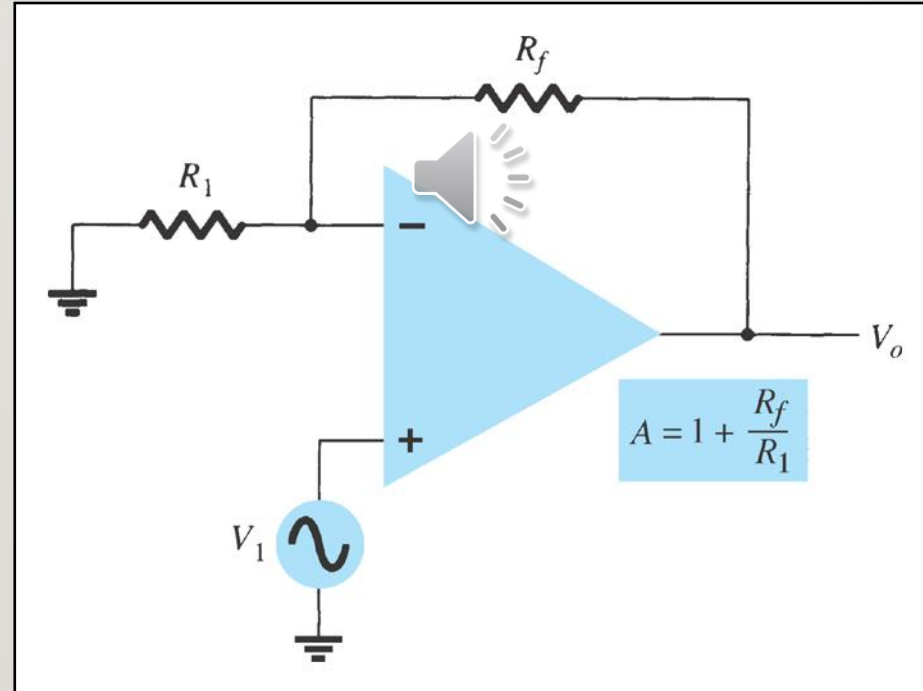

Constant-Gain non inverting Amplifier

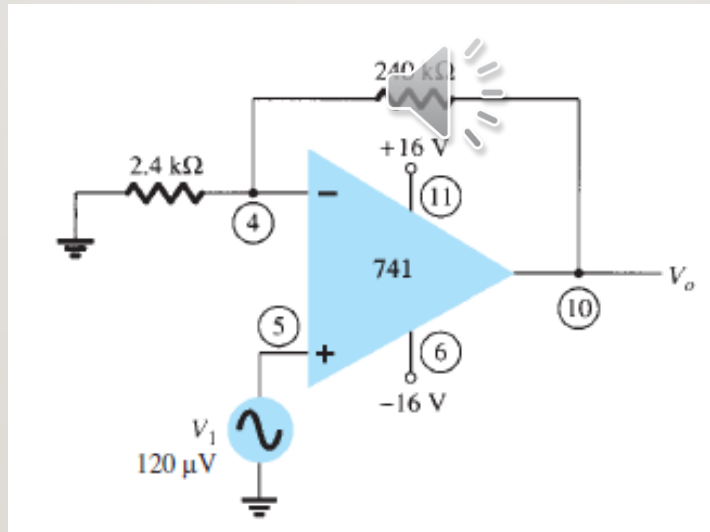Example 11.2: Determine the output voltage of a given circuit for an input voltage of $120\mu\text{V}$



Constant-Gain non inverting Amplifier

Example 11.2 Solution: It is clear from the circuit that it is a constant gain non inverting amplifier so

$$A = 1 + \frac{R_f}{R_1} = 1 + \frac{240 \text{ k}\Omega}{2.4 \text{ k}\Omega} = 1 + 100 = 101$$

The output voltage is then

$$V_o = AV_i = 101(120 \mu\text{V}) = 12.12 \text{ mV}$$




Multiple-Stage Gains

The total gain (3-stages) is given by:

$$A = A_1 A_2 A_3$$


or:
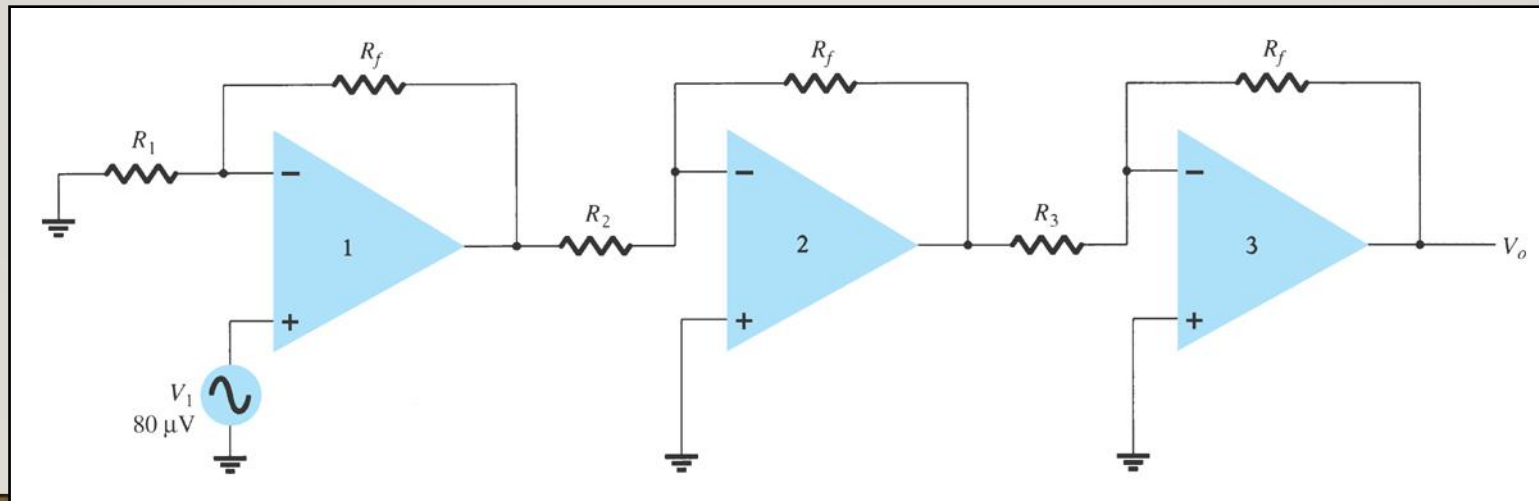
$$A = \left(1 + \frac{R_f}{R_1} \right) \left(-\frac{R_f}{R_2} \right) \left(\frac{R_f}{R_3} \right)$$



Multiple Stage Gain Amplifier

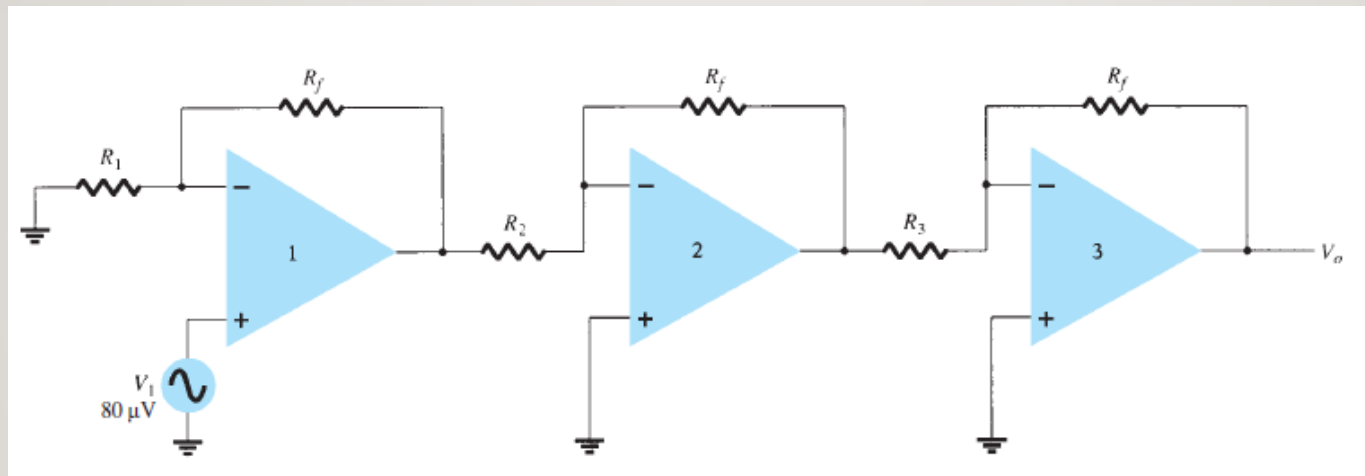Example 11.3: Determine the output voltage using the given circuit below for resistor components of value $R_f = 470\text{k}\Omega$, $R_1 = 4.3\text{k}\Omega$, R_2 and $R_3 = 33\text{k}\Omega$ for an input voltage of $80\mu\text{V}$



Multiple Stage Gain Amplifier

Example 11.3 Solution:

The amplifier gain is calculated to be

$$\begin{aligned} A &= A_1 A_2 A_3 = \left(1 + \frac{R_f}{R_1}\right) \left(-\frac{R_f}{R_2}\right) \left(-\frac{R_f}{R_3}\right) \\ &= \left(1 + \frac{470 \text{ k}\Omega}{4.3 \text{ k}\Omega}\right) \left(-\frac{470 \text{ k}\Omega}{33 \text{ k}\Omega}\right) \left(-\frac{470 \text{ k}\Omega}{33 \text{ k}\Omega}\right) \\ &= (110.3)(-14.2)(-14.2) = 22.2 \times 10^3 \end{aligned}$$

$$V_o = AV_i = 22.2 \times 10^3 (80 \mu\text{V}) = 1.78 \text{ V}$$




Multiple Stage Gain Amplifier

Example 11.4: Show the connection of an LM124 quad op-amp as a three stage amplifier with gains of +10, -18, and -27. Use a $270\text{k}\Omega$ feedback resistor for all three circuits. What output voltage will result for an input voltage of $150\mu\text{V}$



Multiple Stage Gain Amplifier

Example 11.4 Solution:

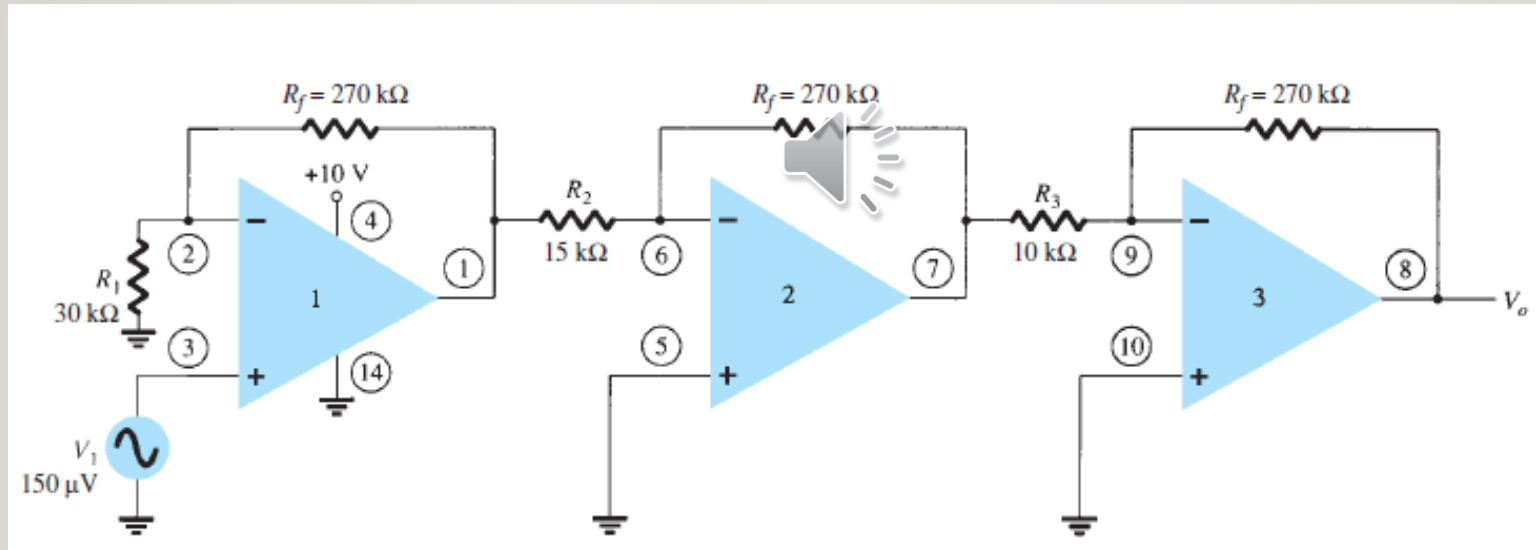

Multiple Stage Gain Amplifier

Example 11.4 Solution:

For the gain of +10,

$$A_1 = 1 + \frac{R_f}{R_1} = +10$$

$$\frac{R_f}{R_1} = 10 - 1 = 9$$

$$R_1 = \frac{R_f}{9} = \frac{270 \text{ k}\Omega}{9} = 30 \text{ k}\Omega$$



For the gain of -18,


$$A_2 = -\frac{R_f}{R_2} = -18$$

$$R_2 = \frac{R_f}{18} = \frac{270 \text{ k}\Omega}{18} = 15 \text{ k}\Omega$$

Multiple Stage Gain Amplifier

Example 11.4 Solution:

For the gain of -27 ,

$$A_3 = -\frac{R_f}{R_3} = -27$$
$$R_3 = \frac{R_f}{27} = \frac{270 \text{ k}\Omega}{27} = 10 \text{ k}\Omega$$


The circuit showing the pin connections and all components used is given in Fig. 11.6. For an input of $V_1 = 150 \mu\text{V}$, the output voltage is

$$V_o = A_1 A_2 A_3 V_1 = (10)(-18)(-27)(150 \mu\text{V}) = 4860(150 \mu\text{V})$$
$$= 0.729 \text{ V}$$

Multiple Stage Gain Amplifier

Example 11.5: Show the connection of an LM348 to provide outputs that are 10, 20 and 50 times larger than the. Use a $200\text{k}\Omega$ feedback resistor for all three stages.



Multiple Stage Gain Amplifier

Example 11.5 Solution:

The resistor component for each stage is calculated to be

$$R_1 = -\frac{R_f}{A_1} = -\frac{500 \text{ k}\Omega}{-10} = 50 \text{ k}\Omega$$


$$R_2 = -\frac{R_f}{A_2} = -\frac{500 \text{ k}\Omega}{-20} = 25 \text{ k}\Omega$$

$$R_3 = -\frac{R_f}{A_3} = -\frac{500 \text{ k}\Omega}{-50} = 10 \text{ k}\Omega$$



Multiple Stage Gain Amplifier


Example 11.5 Solution:

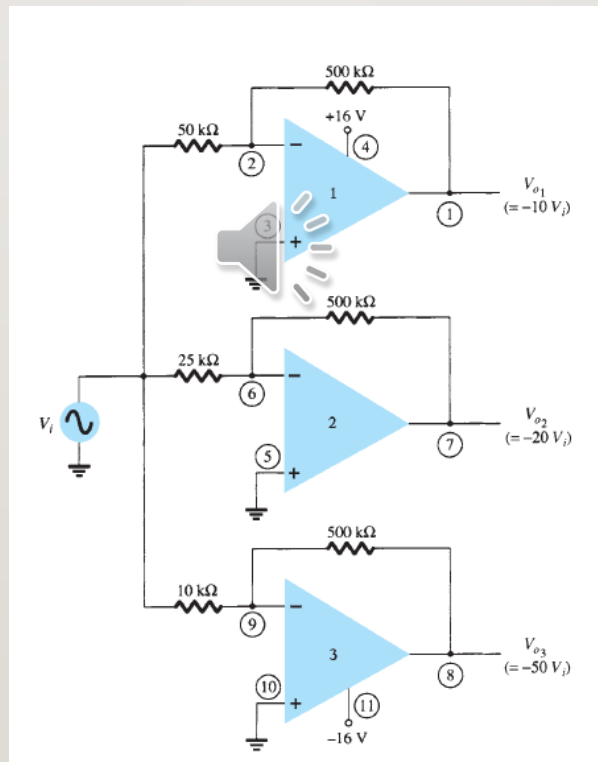

Voltage Summing


The output is the sum of individual signals times the gain:
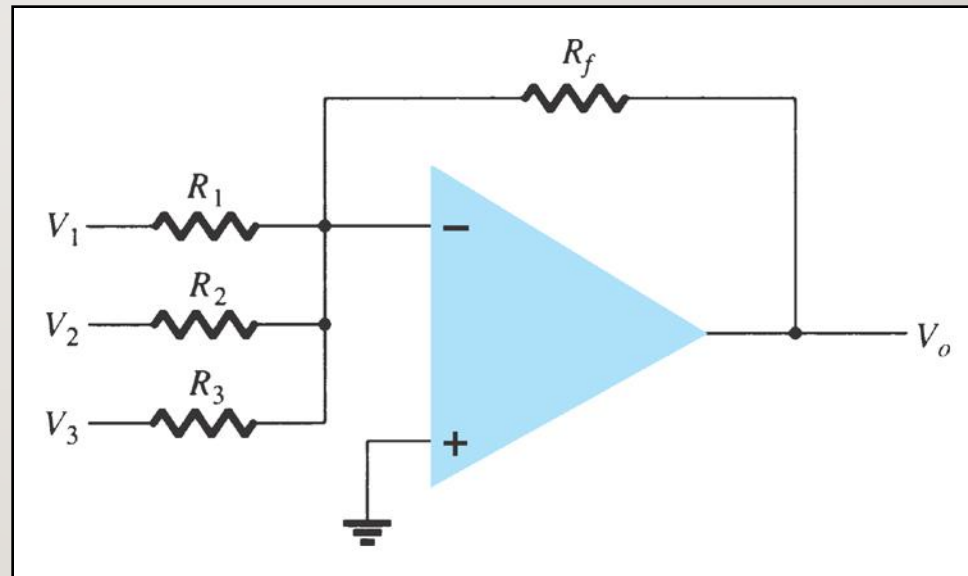
$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$



Voltage Summing Amplifier

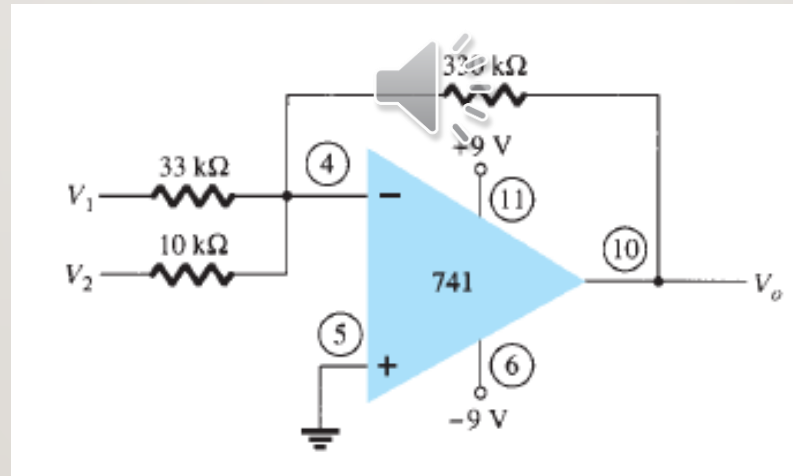Example 11.6: Calculate the output voltage of the given circuit. The inputs are $V_1 = 50\text{mV}\sin(1000t)$ and $V_2 = 10\text{mV}\sin(3000t)$



Voltage Summing Amplifier

Example 11.6 Solution:


The output voltage is

$$\begin{aligned} V_o &= -\left(\frac{330\text{ k}\Omega}{33\text{ k}\Omega}V_1 + \frac{330\text{ k}\Omega}{10\text{ k}\Omega}V_2\right) = -10V_1 - 33V_2 \\ &= -[10(50\text{ mV})\sin(1000t) + 33(10\text{ mV})\sin(3000t)] \\ &= -[0.5\sin(1000t) + 0.33\sin(3000t)] \end{aligned}$$

Voltage Subtractor


Two signals can be subtracted from one another in a number of ways. Figure shows two op-amp stages used to provide subtraction of input signals
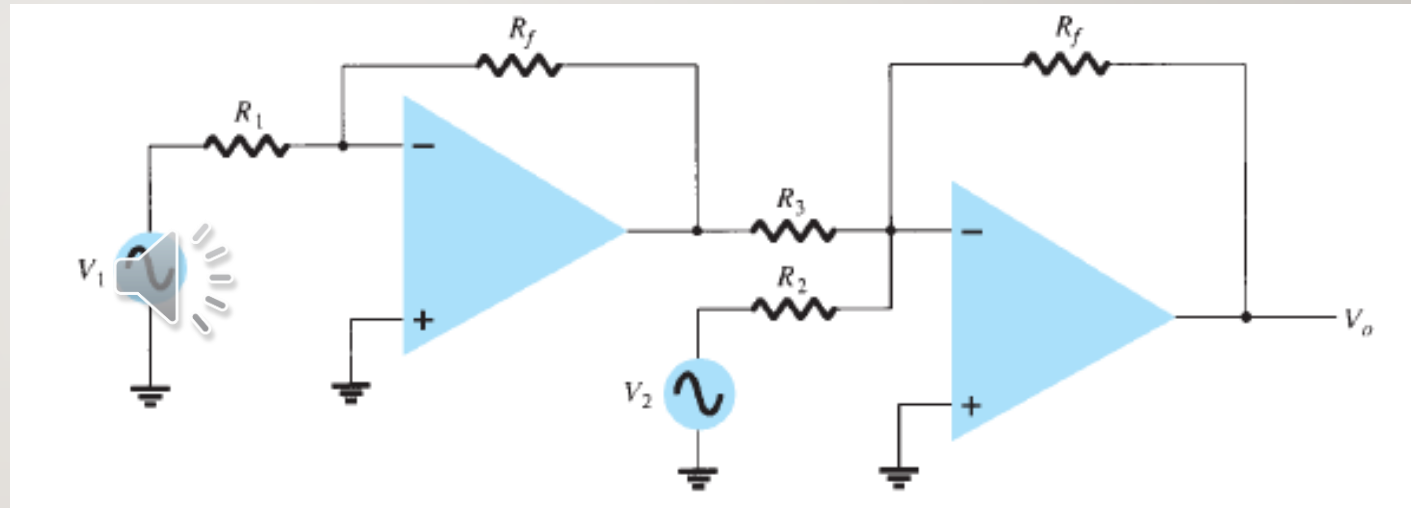
$$V_o = -\left(\frac{R_f}{R_2}V_2 - \frac{R_f}{R_3}\frac{R_f}{R_1}V_1\right)$$



Voltage Subtractor Amplifier

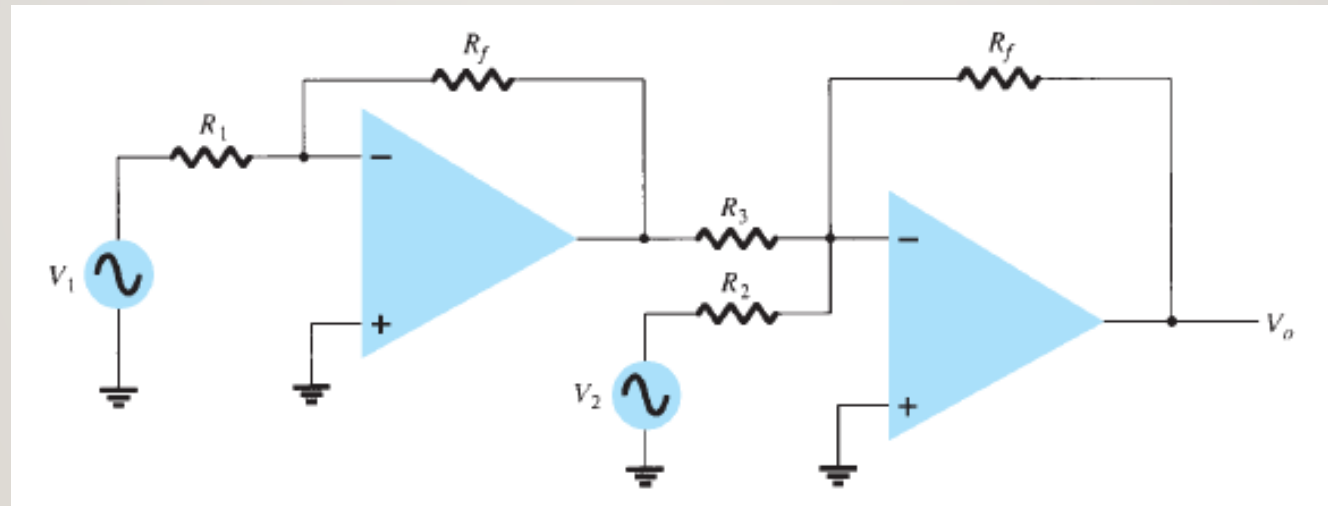Example 11.7: Calculate the output voltage of the given circuit with components $R_f = 1\text{M}\Omega$, $R_1 = 100\text{k}\Omega$, $R_2 = 50\text{k}\Omega$, $R_3 = 500\text{k}\Omega$,



Voltage Subtractor Amplifier


Example 11.7 Solution:

$$V_o = -\left(\frac{1\text{ M}\Omega}{50\text{ k}\Omega}V_2 - \frac{1\text{ M}\Omega}{500\text{ k}\Omega}\frac{1\text{ M}\Omega}{100\text{ k}\Omega}V_1\right) = -(20V_2 - 20V_1) = -20(V_2 - V_1)$$

The output is seen to be the difference of V_2 and V_1 multiplied by a gain factor of -20 .


Voltage Subtractor

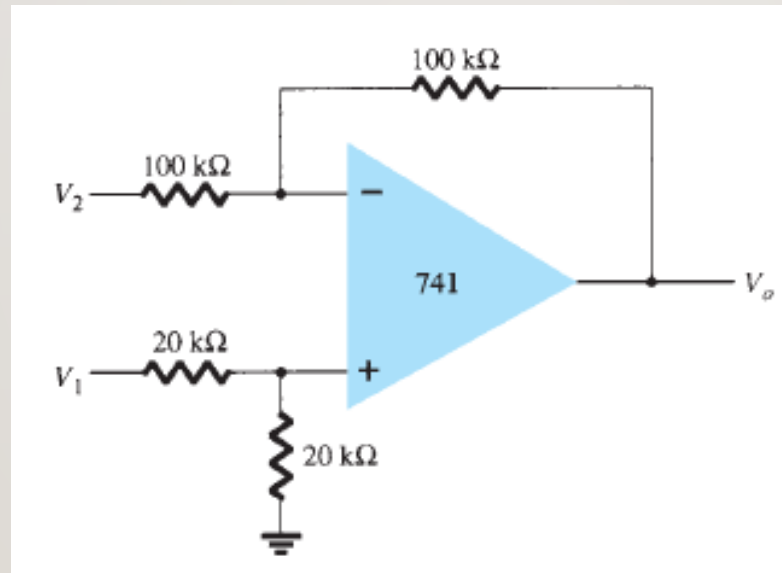Example 11.8: Determine the output voltage of the given circuit



Voltage Subtractor

Example 11.8 Solution:

$$\begin{aligned} V_o &= \left(\frac{20 \text{ k}\Omega}{20 \text{ k}\Omega + 20 \text{ k}\Omega} \right) \left(\frac{100 \text{ k}\Omega + 100 \text{ k}\Omega}{100 \text{ k}\Omega} \right) V_1 - \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega} V_2 \\ &= V_1 - V_2 \end{aligned}$$


The resulting output voltage is seen to be the difference of the two input voltages.