

Lecture 12

Source Transformation

Source Transformation


Basis for Thevenin and Norton Equivalent
Circuits

Source Transformation

- We have noticed that series-parallel combination and wye-delta transformation help simplify circuits.
- Source transformation is another tool for simplifying circuits.
- Basic to these tools is the concept of equivalence.
 - an equivalent circuit is one whose v - i characteristics are identical with the original circuit.

Source Transformation

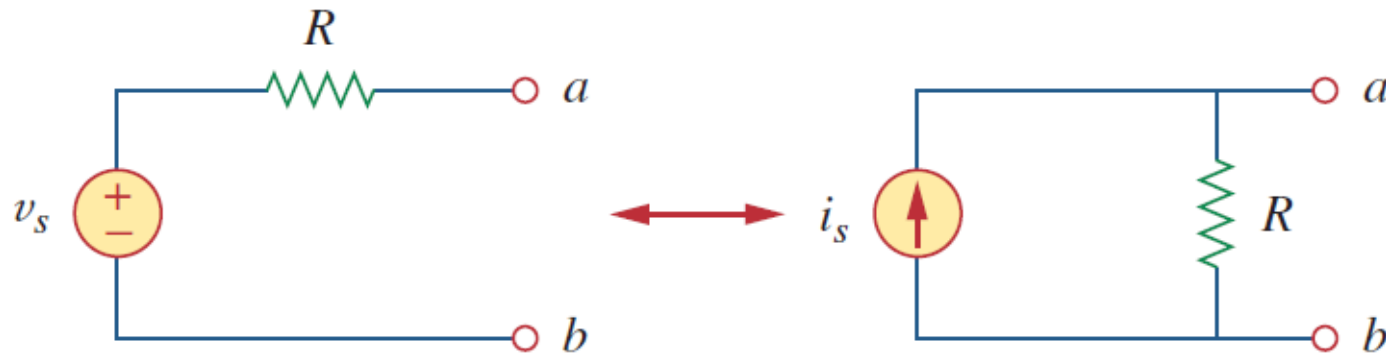
- A **source transformation** is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.



$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

Source Transformation

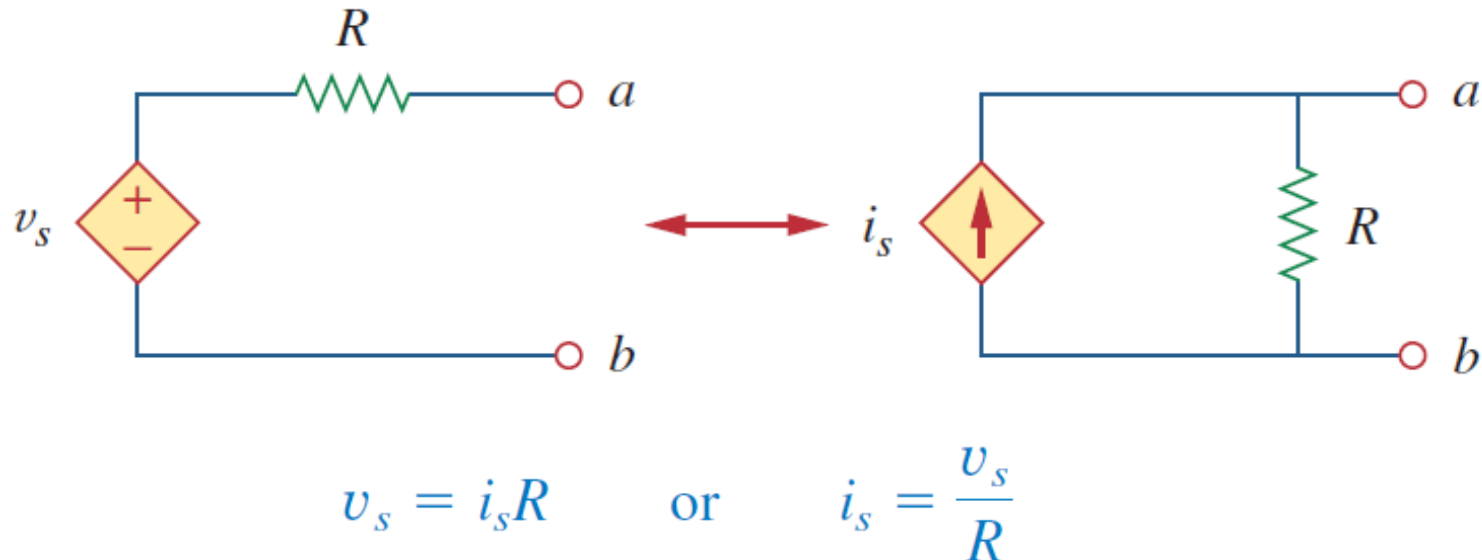- Source transformation also applies to dependent sources, provided we carefully handle the dependent variable.
 - A dependent voltage source in series with a resistor can be transformed to a dependent current source in parallel with the resistor or vice versa.




Equivalence

- An equivalent circuit is one in which the i - v characteristics are identical to that of the original circuit.
 - The magnitude and sign of the voltage and current at a particular measurement point are the same in the two circuits.

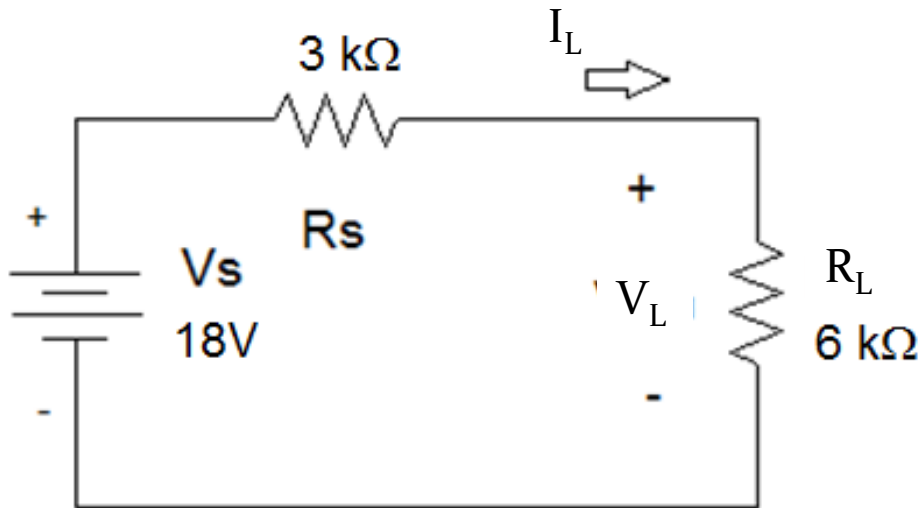
Example 1...

- Find an equivalent current source to replace V_s and R_s in the circuit below.



...Example 1...

- Find I_L and V_L .

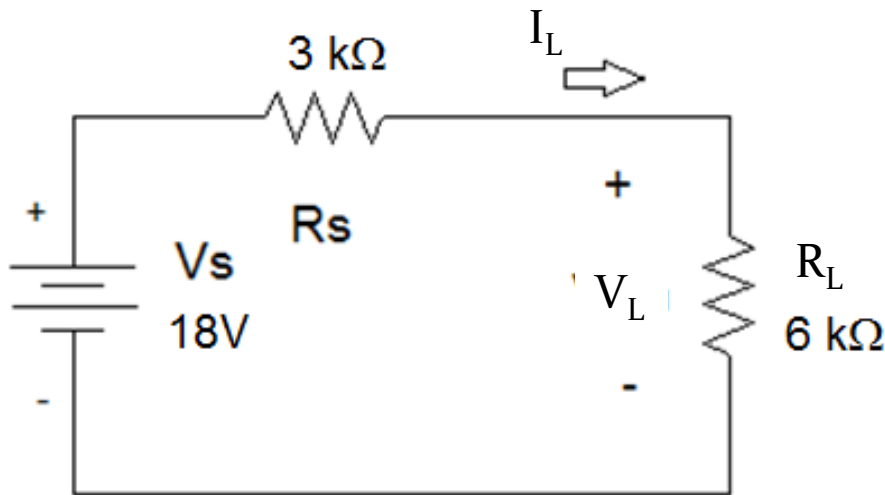

$$V_L = \frac{R_L}{R_L + R_s} V_s$$

$$V_L = \frac{6\text{ k}\Omega}{6\text{ k}\Omega + 3\text{ k}\Omega} 18V = 12V$$

$$I_L = V_L / R_L$$

$$I_L = 12V / 6\text{ k}\Omega = 2\text{ mA}$$


$$P_{V_s} = P_L + P_{R_s}$$

$$P_{V_s} = 12V(2\text{ mA}) + (18V - 12V)(2\text{ mA})$$

$$P_{V_s} = 36\text{ mW}$$

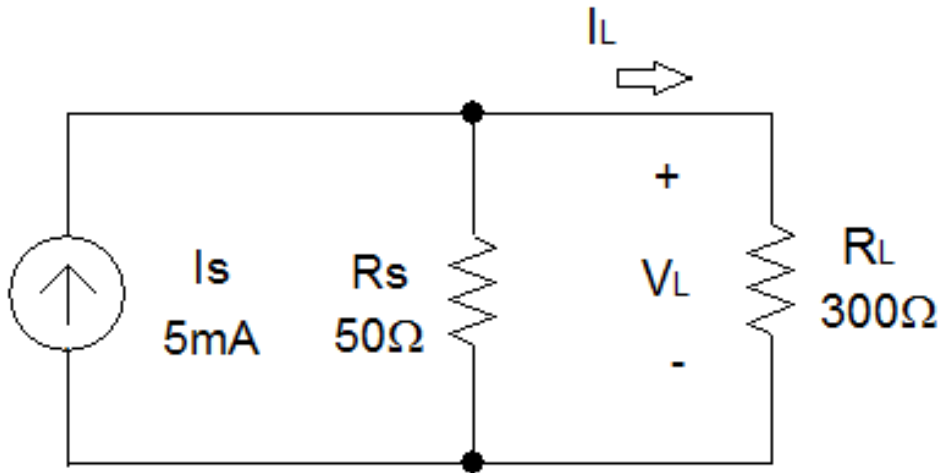
Example 2...

- Find an equivalent voltage source to replace I_s and R_s in the circuit below.



...Example 2...

- Find I_L and V_L .

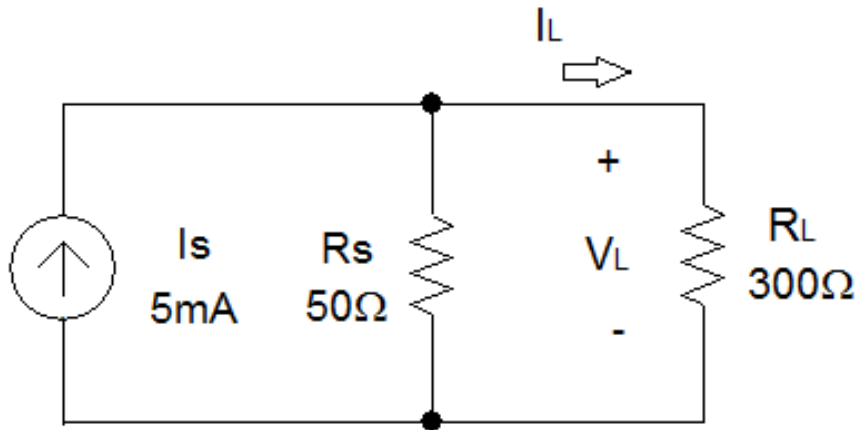

$$I_L = \frac{50\Omega}{300\Omega + 50\Omega} I_s$$

$$I_L = 0.714\text{mA}$$

$$V_L = I_L R_L$$

$$V_L = 0.714\text{mA}(300\Omega) = 0.214\text{V}$$

$$P_{V_s} = P_L + P_{R_s}$$



$$P_{V_s} = 0.214\text{V}(0.714\text{mA})$$

$$+ 0.214\text{V}(5\text{mA} - 0.714\text{mA})$$

$$P_{V_s} = 1.07\text{mW}$$

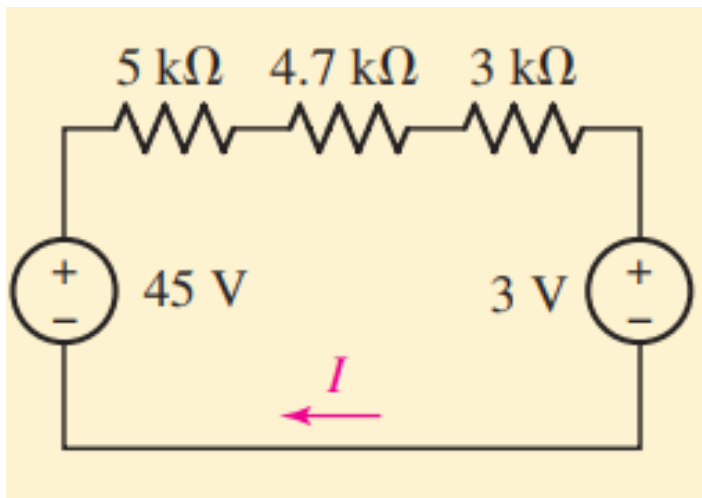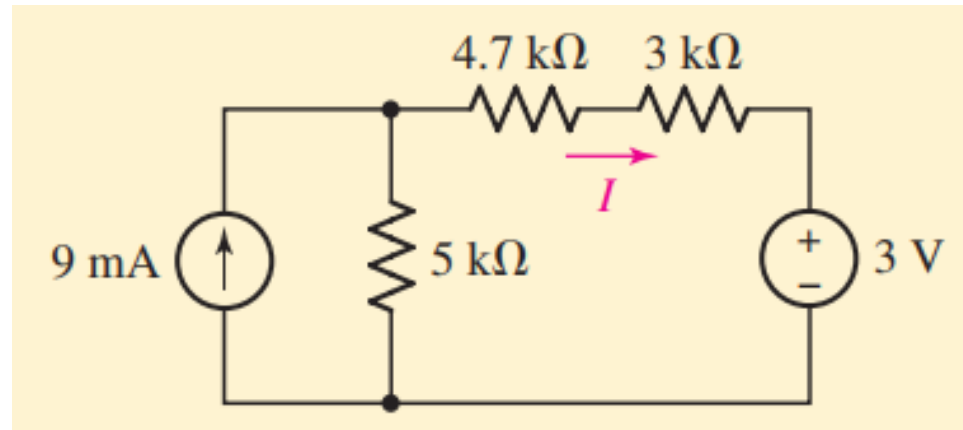Example 3





Compute the current through the $4.7\text{ k}\Omega$ resistor in Fig. 5.17a after transforming the 9 mA source into an equivalent voltage source.



$$-45 + 5000I + 4700I + 3000I + 3 = 0$$

which is easily solved to yield $I = 3.307\text{ mA}$.

Example 4

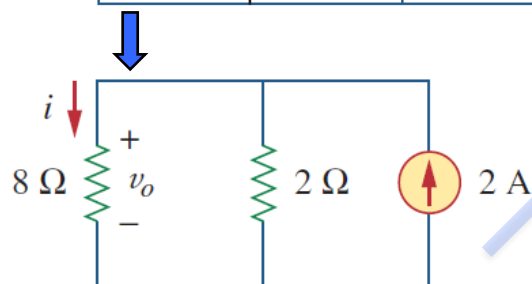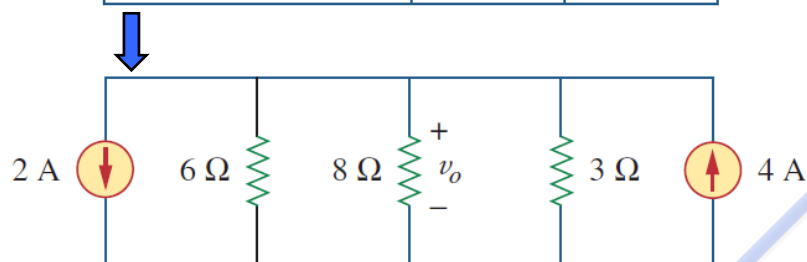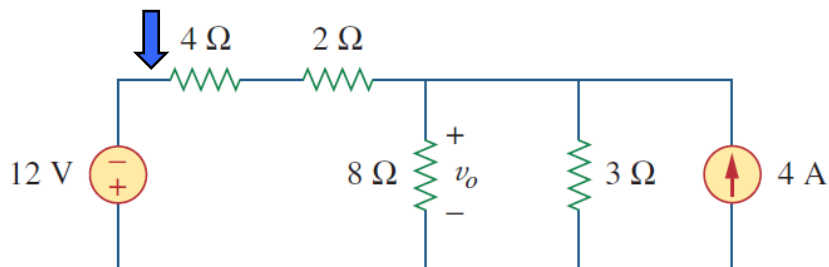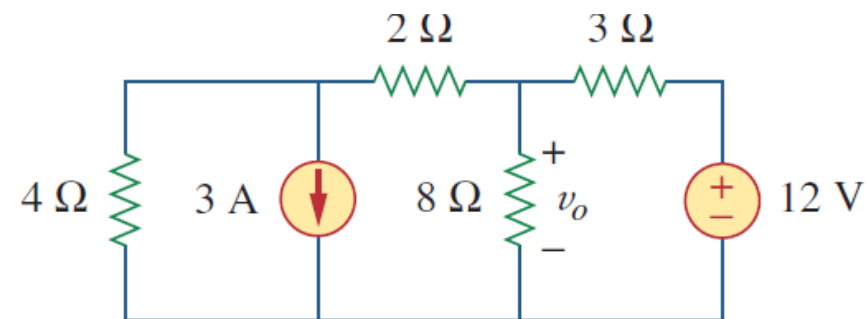

- Use source transformation to find v_o in the circuit.

– Use current division

$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$



$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$


– or

$$v_o = (8 \parallel 2)(2 \text{ A}) = \frac{8 \times 2}{10}(2) = 3.2 \text{ V}$$

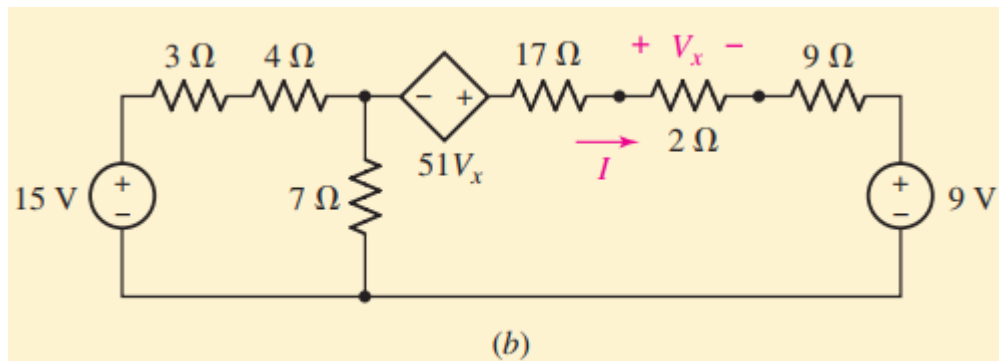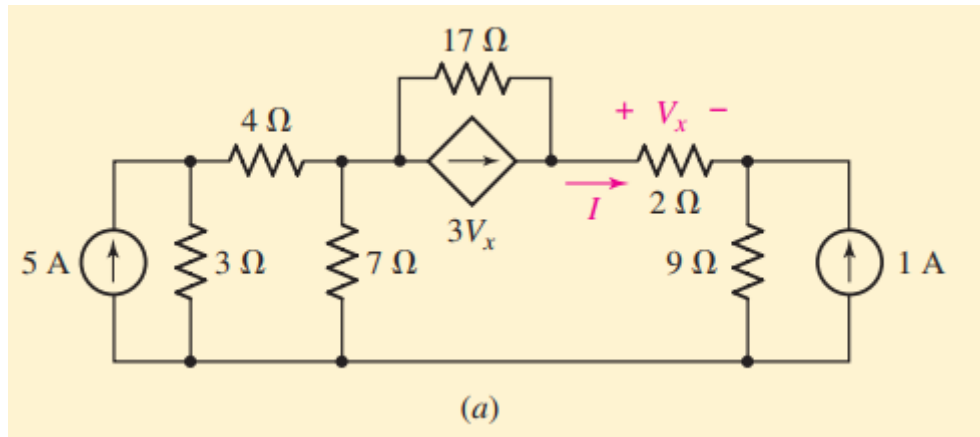
Example 5

Calculate the current through the $2\ \Omega$ resistor in Fig. 5.19a by making use of source transformations to first simplify the circuit.



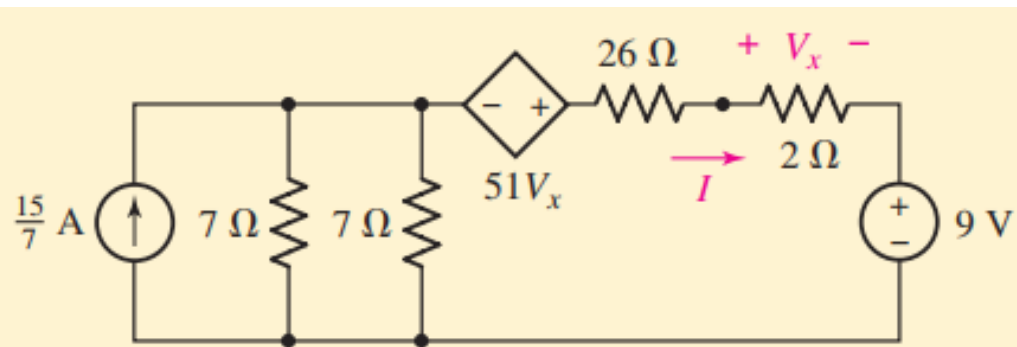

(c)

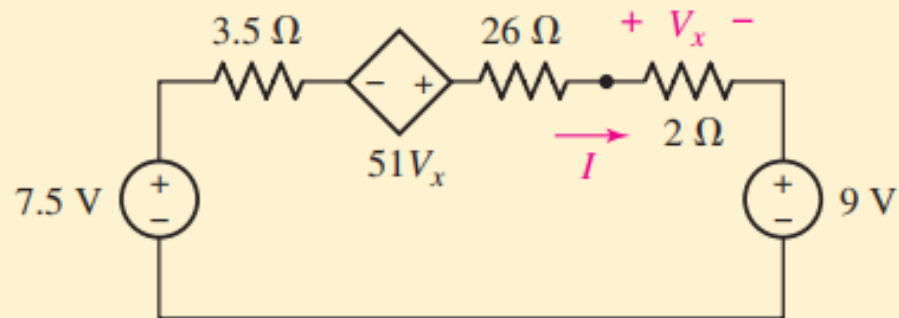

(d)

The current I can now be found using KVL:

$$-7.5 + 3.5I - 51V_x + 28I + 9 = 0$$

where

$$V_x = 2I$$


Thus,

$$I = 21.28\text{ mA}$$

Example 6

- Use source transformation to find i_0 in the circuit.

Answer: 1.78 A.

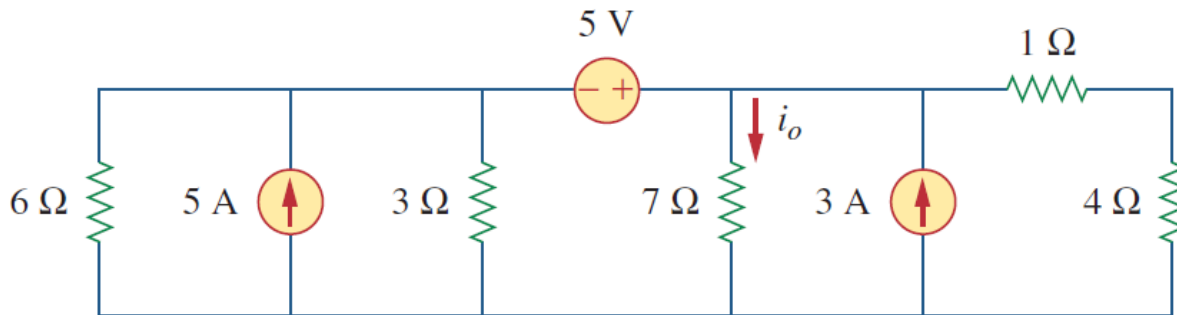

Thank You