

# Common Op-Amp Circuits

---

Inverting amplifier

Noninverting amplifier

Unity follower

Summing amplifier

Integrator

Differentiator






# Inverting Op-Amp

The input signal is applied to the **inverting (–) input**

The **non-inverting input (+)** is grounded

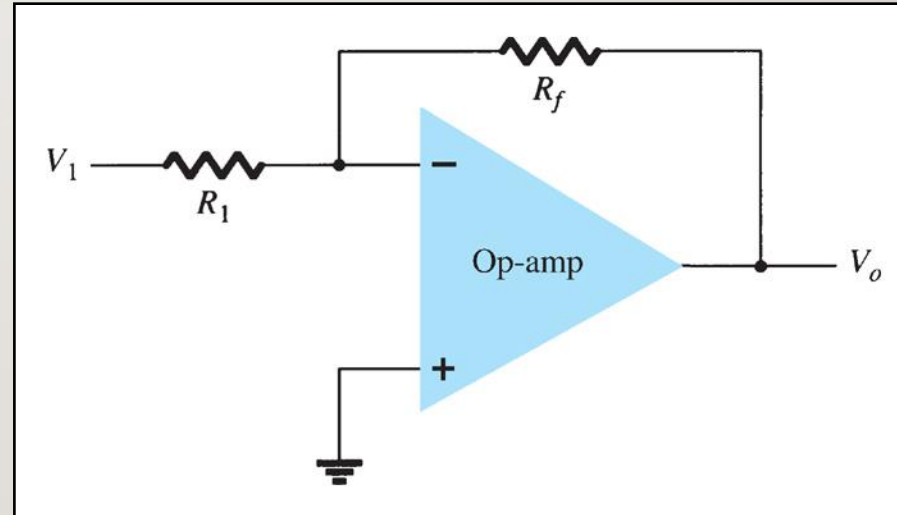The **feedback resistor** ( $R_f$ ) is connected from the output to the negative (inverting) input; providing **negative feedback**.



# Inverting Op-Amp Gain

Gain is set using external resistors:  $R_f$  and  $R_1$


$$A_v = \frac{V_o}{V_i} = \frac{R_f}{R_1}$$

Gain can be set to any value by manipulating the values of  $R_f$  and  $R_1$ .

Unity gain ( $A_v = 1$ ):

$$R_f = R_1$$

$$A_v = \frac{-R_f}{R_1} = -1$$

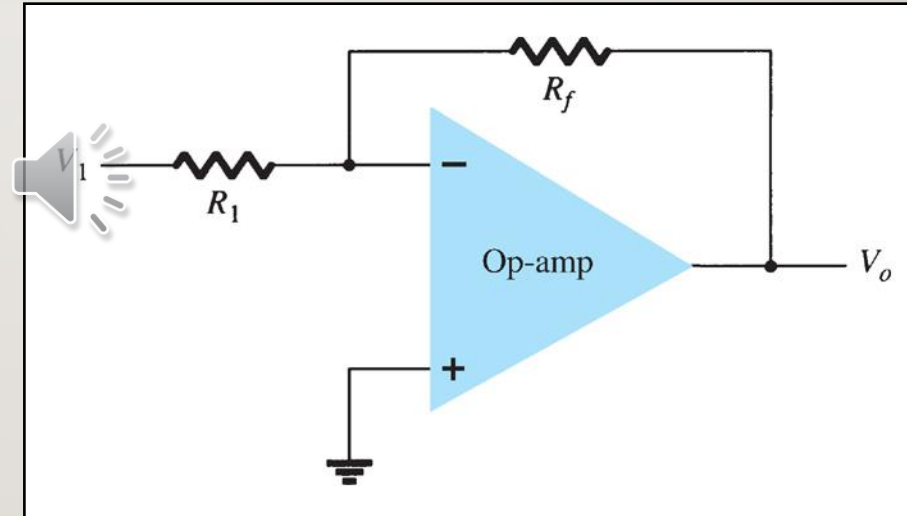

The negative sign denotes a  $180^\circ$  phase shift between input and output.

# Inverting Amplifier

---

Example 10.5: If  $R_f = 500\text{k}\Omega$  and  $R_1 = 100\text{k}\Omega$ , what output voltage results for an input of  $V_1 = 2\text{V}$

Solution:


$$V_o = -\frac{R_f}{R_1} V_1 = -\frac{500\text{ k}\Omega}{100\text{ k}\Omega} (2\text{ V}) = -10\text{ V}$$

# Non Inverting Op-Amp Gain

Gain is set using external resistors:  $R_f$  and  $R_1$

$$A_v = \left(1 + \frac{R_f}{R_1}\right)$$

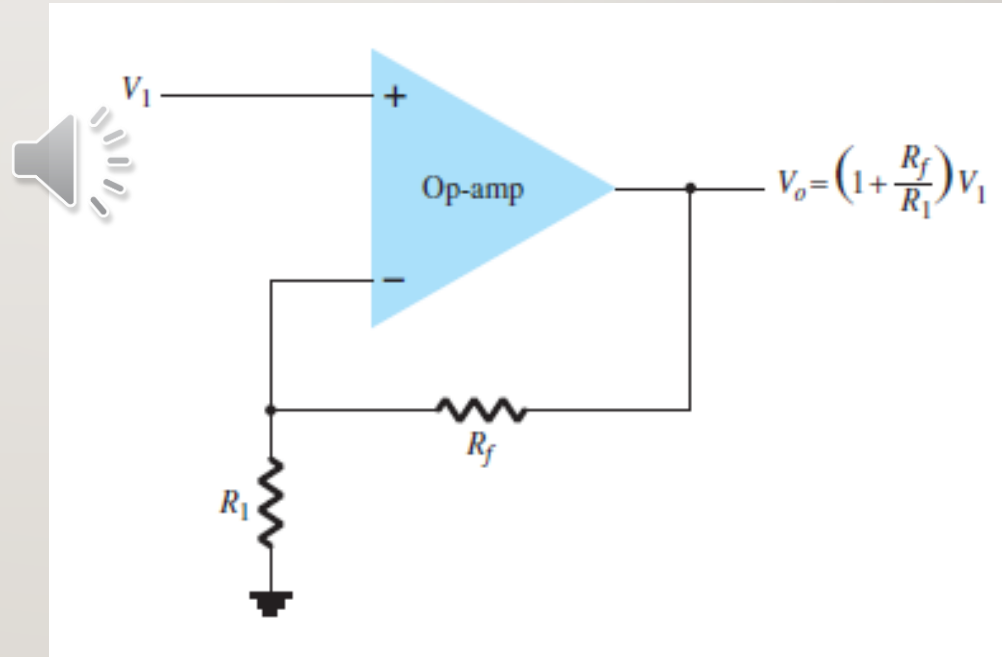Gain can be set to any value by manipulating the values of  $R_f$  and  $R_1$ .





# Non Inverting Amplifier

---

Example 10.6: Calculate the output voltage of a noninverting op-amp for values  $V_1 = 2\text{V}$ ,  $R_f = 500\text{k}\Omega$  and  $R_1 = 100\text{k}\Omega$

Solution:




$$V_o = \left(1 + \frac{R_f}{R_1}\right)V_1 = \left(1 + \frac{500\text{ k}\Omega}{100\text{ k}\Omega}\right)(2\text{ V}) = 6(2\text{ V}) = +12\text{ V}$$

# Unity Follower

---


$$V_o = V_1$$

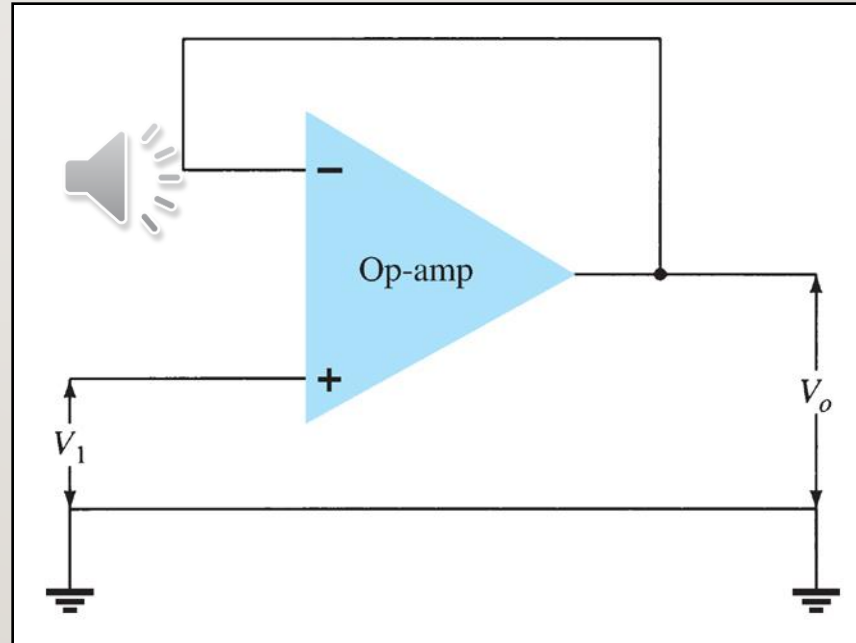
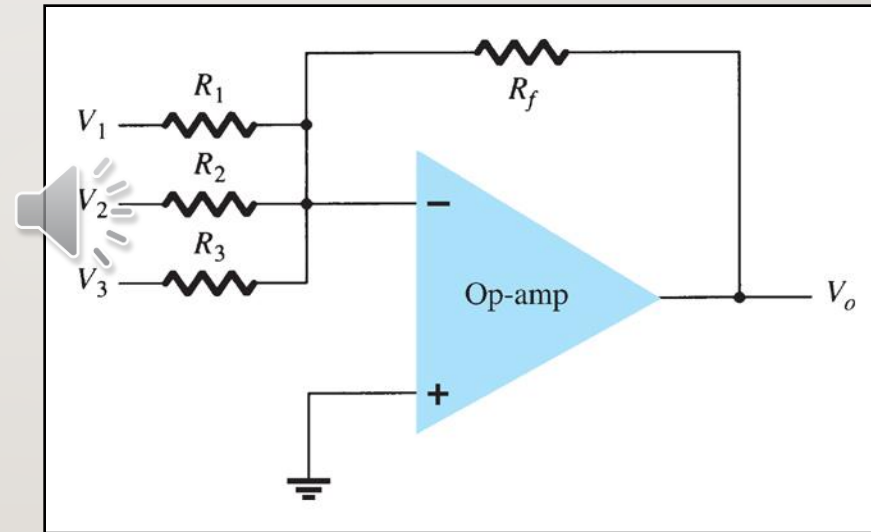
# Summing Amplifier

Because the op-amp has a high input impedance, the multiple inputs are treated as separate inputs.

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$





# Summing Amplifier

Example 10.7: Calculate the output voltage of an op-amp summing amplifier for the following set of voltages. Use  $R_f = 1\text{ M}\Omega$  in all cases.

---

- a.  $V_1 = +1\text{ V}$ ,  $V_2 = +2\text{ V}$ ,  $V_3 = +3\text{ V}$ ,  $R_1 = 500\text{ k}\Omega$ ,  $R_2 = 1\text{ M}\Omega$ ,  $R_3 = 1\text{ M}\Omega$ .  
b.  $V_1 = -2\text{ V}$ ,  $V_2 = +3\text{ V}$ ,  $V_3 = +1\text{ V}$ ,  $R_1 = 200\text{ k}\Omega$ ,  $R_2 = 500\text{ k}\Omega$ ,  $R_3 = 1\text{ M}\Omega$ .





Solution:

$$\begin{aligned}\text{a. } V_o &= -\left[ \frac{1000\text{ k}\Omega}{500\text{ k}\Omega} (+1\text{ V}) + \frac{1000\text{ k}\Omega}{1000\text{ k}\Omega} (+2\text{ V}) + \frac{1000\text{ k}\Omega}{1000\text{ k}\Omega} (+3\text{ V}) \right] \\ &= -[2(1\text{ V}) + 1(2\text{ V}) + 1(3\text{ V})] = -7\text{ V} \\ \text{b. } V_o &= -\left[ \frac{1000\text{ k}\Omega}{200\text{ k}\Omega} (-2\text{ V}) + \frac{1000\text{ k}\Omega}{500\text{ k}\Omega} (+3\text{ V}) + \frac{1000\text{ k}\Omega}{1000\text{ k}\Omega} (+1\text{ V}) \right] \\ &= -[5(-2\text{ V}) + 2(3\text{ V}) + 1(1\text{ V})] = +3\text{ V}\end{aligned}$$
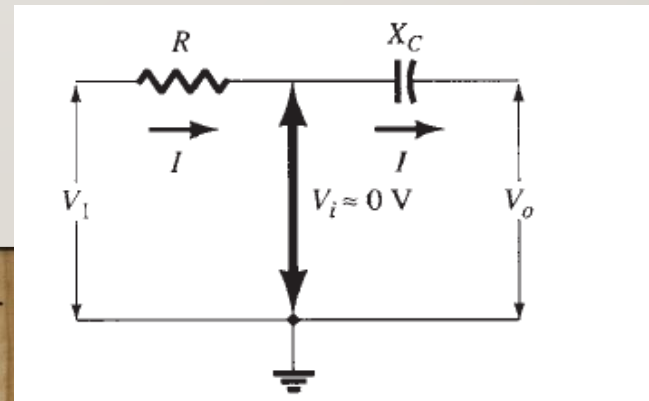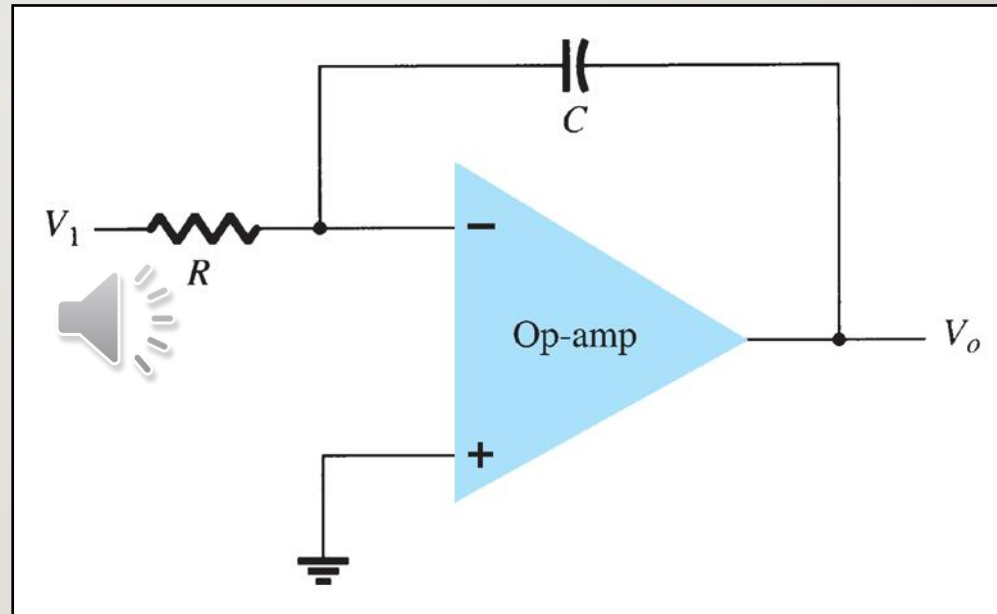
# Integrator

The output is the integral of the input; i.e., proportional to the area under the input waveform. This circuit is useful in low-pass filter circuits and sensor conditioning circuits.


$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$



# Differentiator


The differentiator takes the derivative of the input. This circuit is useful in high-pass filter circuits.

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

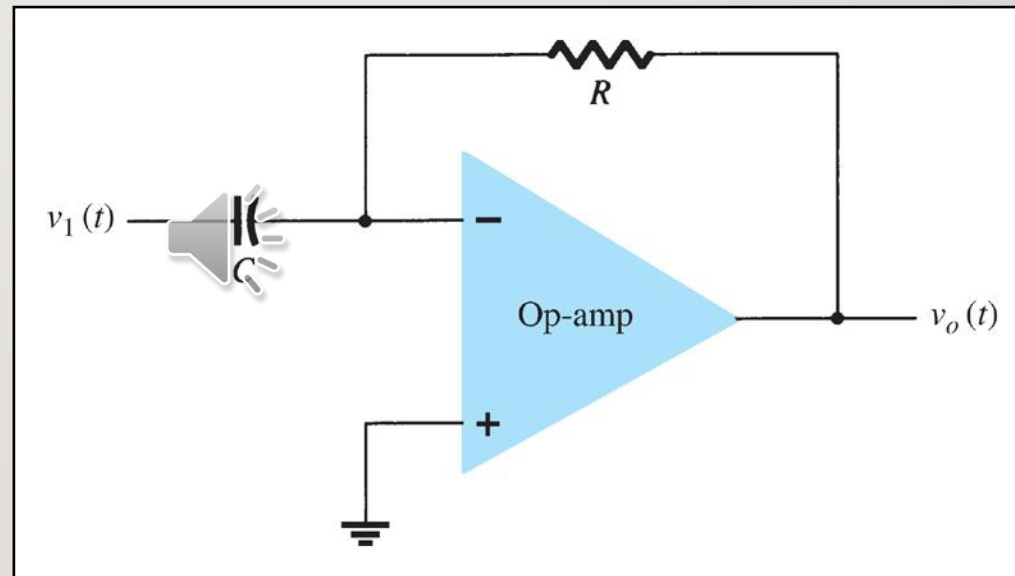
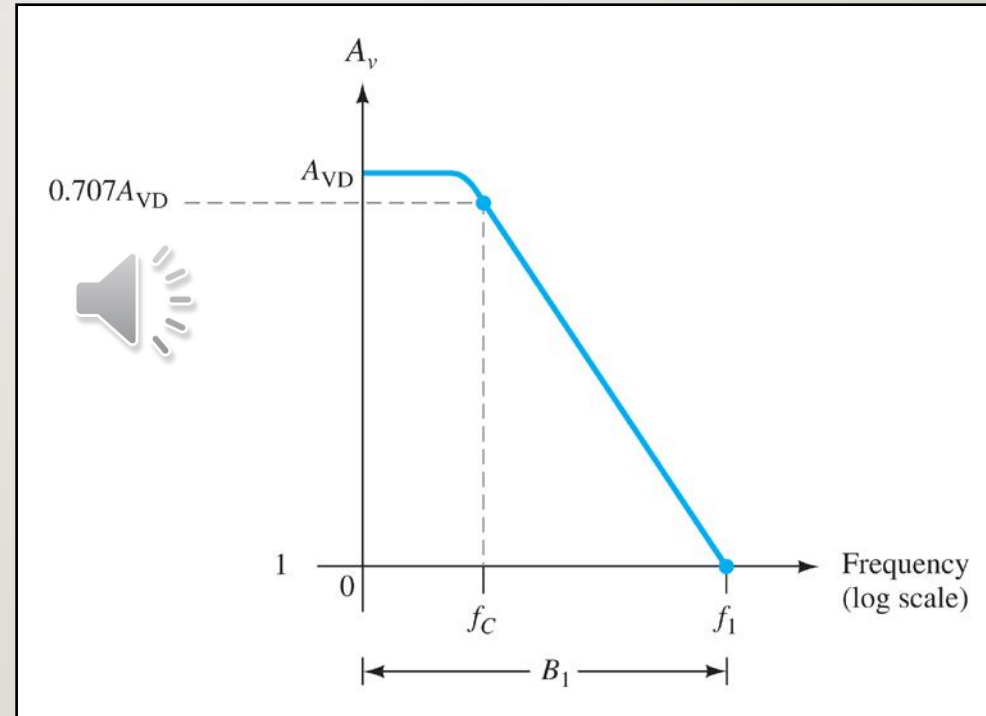
# Gain and Bandwidth

The op-amp's high frequency response is limited by its internal circuitry. The plot shown is for an open loop gain ( $A_{OL}$  or  $A_{VD}$ ). This means that the op-amp is operating at the highest possible gain with no feedback resistor.



In the open loop mode, an op-amp has a narrow bandwidth. The bandwidth widens in closed-loop mode, but the gain is lower.

# Slew Rate (SR)

---

**Slew rate (SR):** The maximum rate at which an op-amp can change output without distortion.


$$SR = \frac{\Delta V_o}{\Delta t} \quad (\text{in V}/\mu\text{s})$$


The SR rating is listed in the specification sheets as the V/μs rating.



# Maximum Signal Frequency

---

The slew rate determines the highest frequency of the op-amp without distortion.


$$f \leq \frac{SR}{2\pi V_p}$$

where  $V_p$  is the peak voltage

# Frequency Parameters

---

An op-amp is a wide-bandwidth amplifier. The following factors affect the bandwidth of the op-amp:



**Gain**

**Slew rate**

# Absolute Ratings

---

These are  
common  
maximum ratings  
for the op-amp.

## *Absolute Maximum Ratings*

Supply voltage	$\pm 22$ V
Internal power dissipation	500 mW
Differential input voltage	$\pm 30$ V
Input voltage	$\pm 15$ V

# Electrical Characteristics

*$\mu A741$  Electrical Characteristics:  $V_{CC} = \pm 15\text{ V}$ ,  $T_A = 25^\circ\text{C}$*


Characteristic	Minimum	Typical	Maximum	Unit
$V_{IO}$ Input offset voltage		1	6	mV
$I_{IO}$ Input offset current		20	200	nA
$I_{IB}$ Input bias current		80	500	nA
$V_{ICR}$ Common-mode input voltage range	$\pm 12$	$\pm 13$		V
$V_{OM}$ Maximum peak output voltage swing	$\pm 12$	$\pm 14$		V
$A_{VD}$ Large-signal differential voltage amplification	20	200		V/mV
$r_i$ Input resistance	0.3	2		$M\Omega$
$r_o$ Output resistance		75		$\Omega$
$C_i$ Input capacitance		1.4		pF
CMRR Common-mode rejection ratio	70	90		dB
$I_{CC}$ Supply current		1.7	2.8	mA
$P_D$ Total power dissipation		50	85	mW

**Note:** These ratings are for specific circuit conditions, and they often include minimum, maximum and typical values.


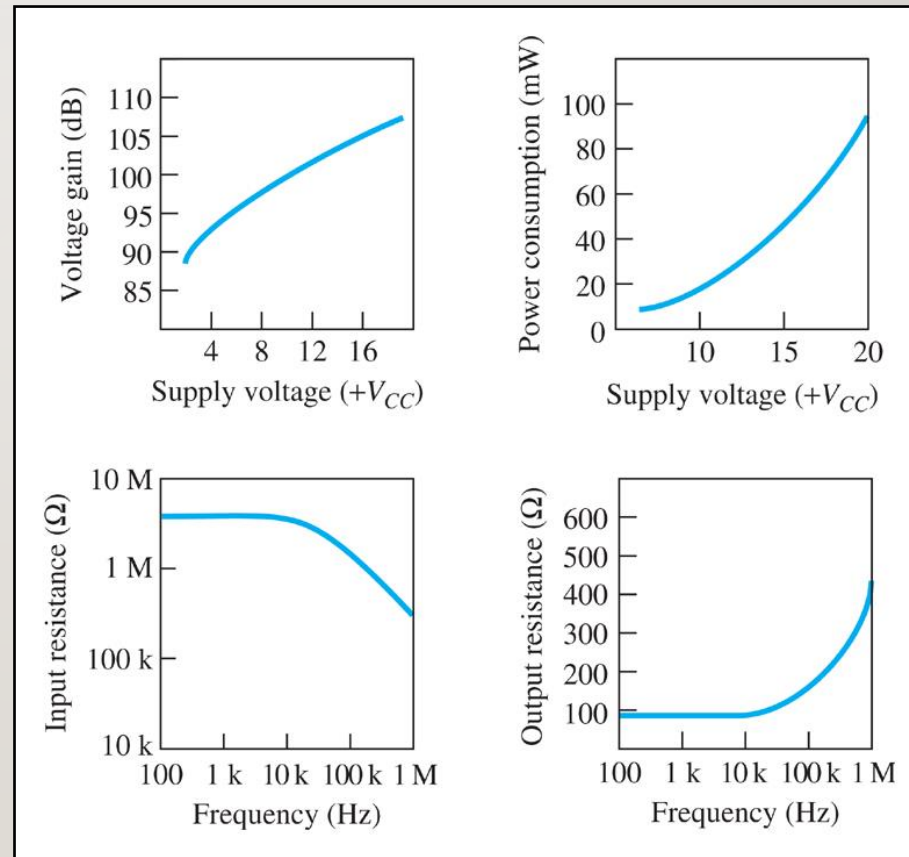
# Op-Amp Performance

The specification sheets will also include graphs that indicate the performance of the op-amp over a wide range of conditions.





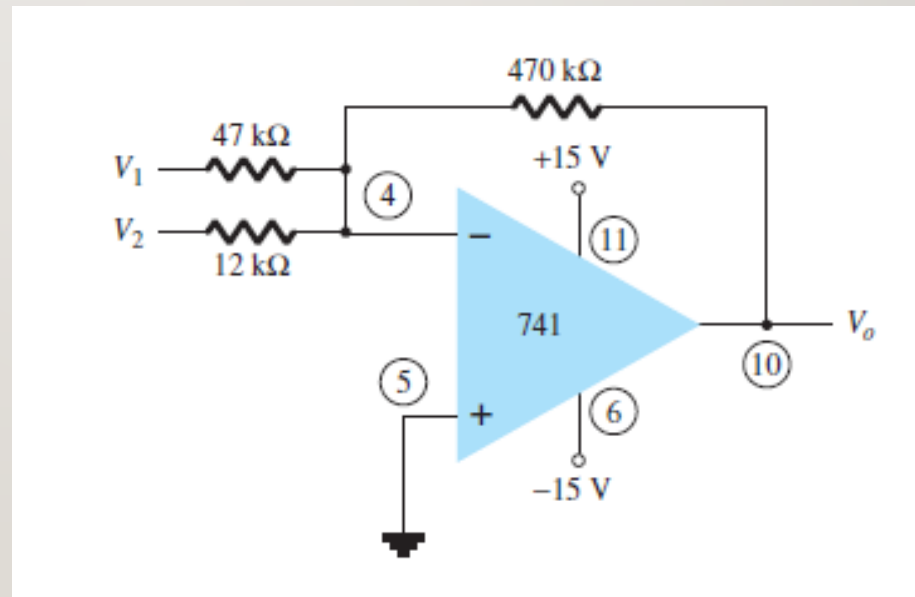
# ASSIGNMENT TASK

---

Analyse the Op Amp configuration to calculate the output voltage for the circuit of Figure below with inputs of  $V_1 = 40 \text{ mV rms}$  and  $V_2 = 20 \text{ mV rms}$ .



# ASSIGNMENT TASK

---

- Analyze the op Amp circuit to determine the output voltage for the circuit of Figure below .

