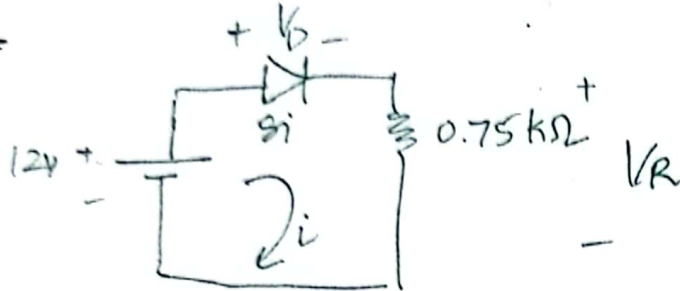


EDC Assignment #1

FA22-BCE-014
Maryam Asif

Q1
find I_D , V_D , and V_R

SS



Calculating I_D and V_D for line of intersection.

KVL

$$-12 + 0.75(1000)i = 0$$

$$i_D = 0.016 = 16 \text{ mA}$$

When $i_D = 0 \text{ A}$


$$V_D = 12 \text{ V}$$

$$V_{DQ} = 0.86 \text{ V}$$

$$I_{DQ} = 15 \text{ mA}$$

↳ voltage across the diode


↳ current across diode

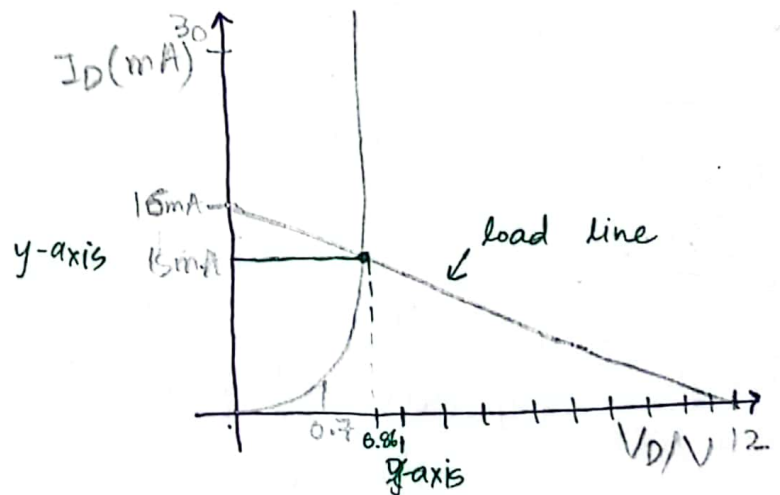

Voltage across Resistor = $V_R = V_S - V_{DQ} = 12 - 0.86 = 11.14 \text{ V}$

Q2

a) Identify the voltage

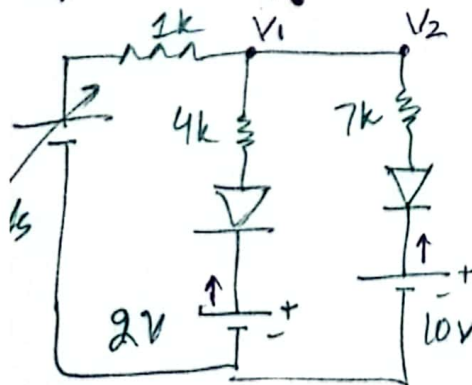

Voltage at node V_0

$$V_0 = V_1 - 2 \text{ V}$$

V_0 Voltage at node 2

$$V_0 = V_2 - 10 \text{ V}$$


Hence, the voltage across V_1 to turn the D_1 on is 2.7 whereas for V_2 is 10.7, since they are in parallel we will apply 10.7V as V_0 .

$$V_s = V_R + 10.7V$$

voltage across the $1k\Omega$ resistor

$$V_s \approx 12V$$

b) find I_{D1} & I_{D2} when $V_s = 20V$

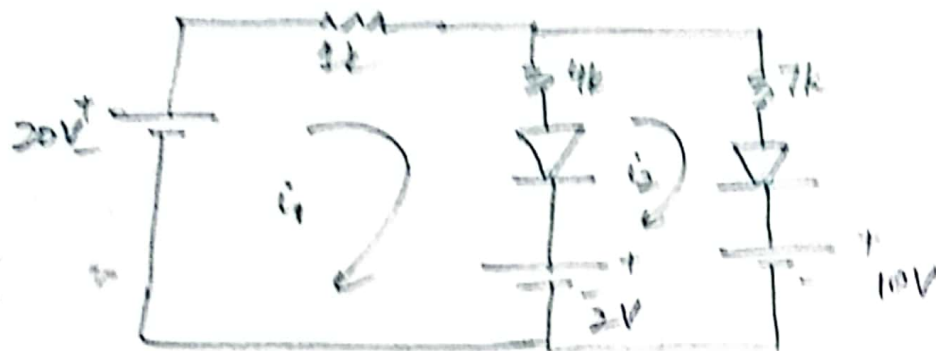

Using Mesh Analysis

Loop 1 eq

$$-20 + 1000i_1 + 4000(i_1 - i_2) + 0.7 + 2 = 0$$

$$-20 + 1000i_1 + 4000i_1 - 4000i_2 + 0.7 + 2 = 0$$

$$5000i_1 - 4000i_2 = 17.3$$

Loop 2 eq

$$-2 + 0.7 + 4000(i_2 - i_1) + 7000i_2 + 0.7 + 10 = 0$$

$$-2 + 0.7 + 4000i_2 - 4000i_1 + 7000i_2 + 0.7 + 10 = 0$$

$$-4000i_1 + 11000i_2 = -9.48$$

$$i_1 = 5.04 \text{ mA}$$

$$i_2 = 1.79 \times 10^{-3} \text{ A} = 1.79 \text{ mA}$$



$$i_1 = 4.05 \text{ mA}$$

$$i_2 = 0.749 \text{ mA}$$

correct
 $I_{D1} = i_1 - i_2 = 3.3 \text{ mA}$

$$I_{D2} = 0.749 \text{ mA}$$

Sketch V_o , and dc voltage 9.2

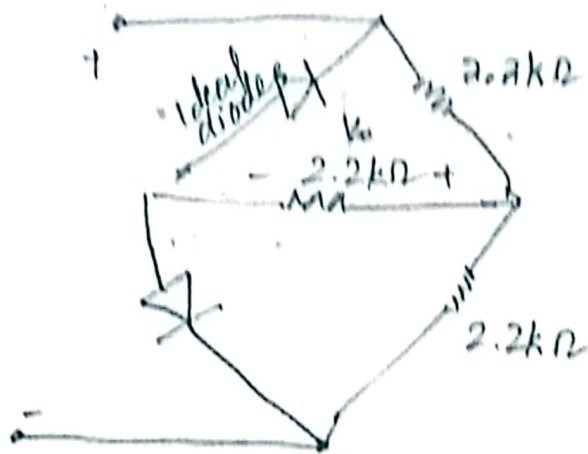
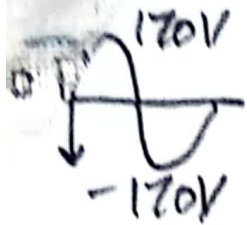


for positive cycle

$$V_{\text{total}} = 1 \div \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$= 1 \div \left(\frac{1}{2200} + \frac{1}{2200} \right) = 1100\Omega$$

Hence

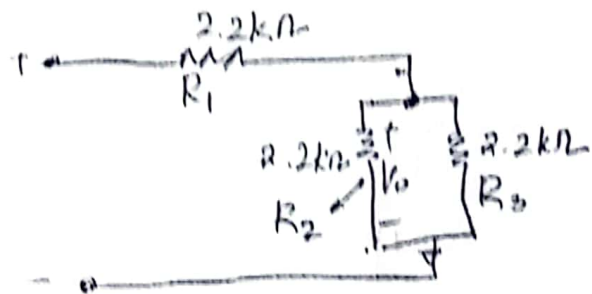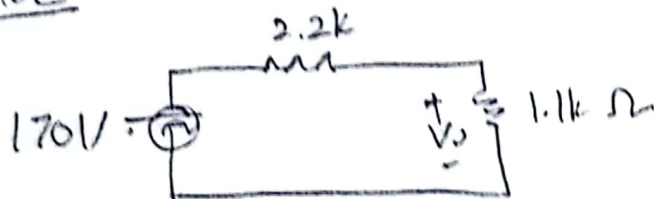


applying Voltage divider



$$V_o = \frac{1.1 \times 1000}{1100 + 2200} \times 170 = \boxed{56.67V}$$

for negative cycle
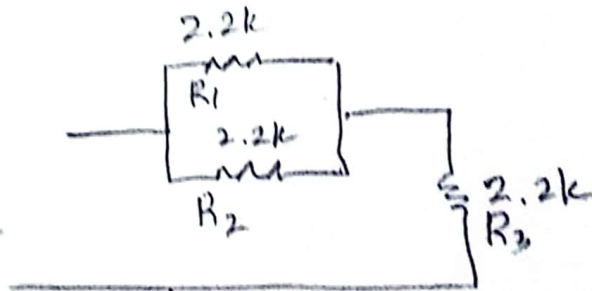
$$V_{\text{total}} = 1 \div \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = 1100\Omega$$



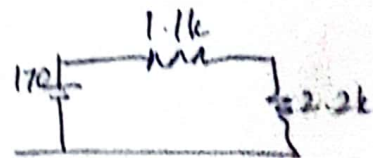
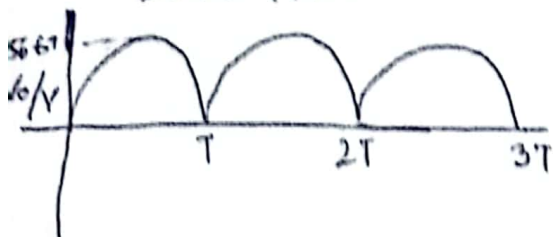
$$V_o = \frac{1100}{2200 + 1100} \times 170 = \boxed{56.67V}$$




$$V_{dc} = 0.636 \times V_0 = 0.636 \times 56.67$$

$$V_{dc} = 36.04V$$

Q4. compute & sketch V_0

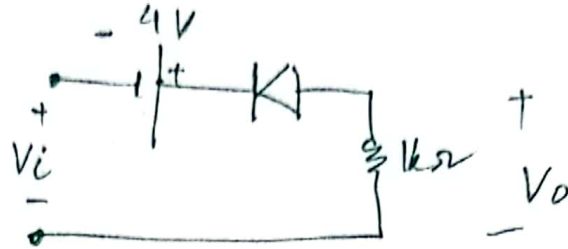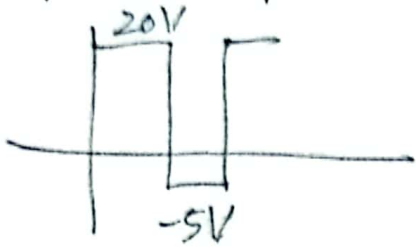

for +ve cycle
circuit

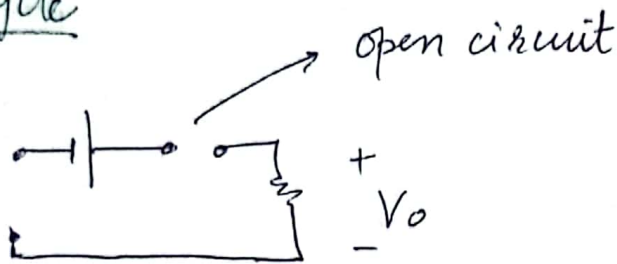


Hence

$$V_0 = 0V$$


for -ve cycle

circuit


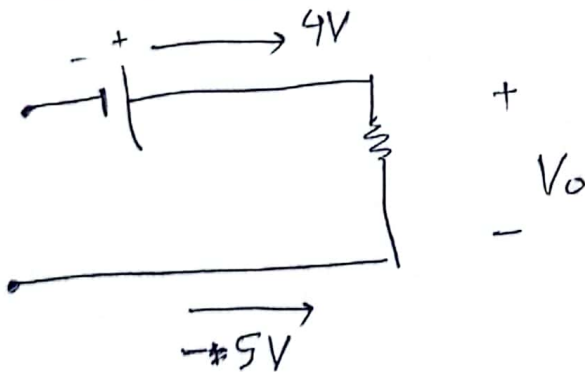


Hence
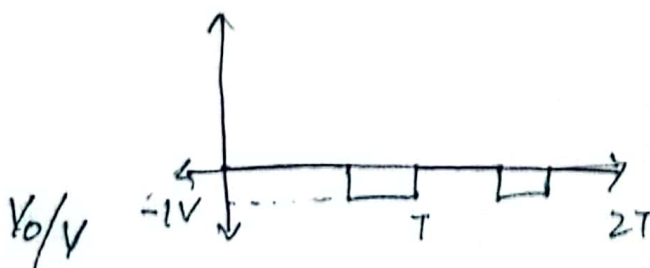
$$V_0 = V_s - V_{\text{internal}} = -5 + 4 = -1V$$



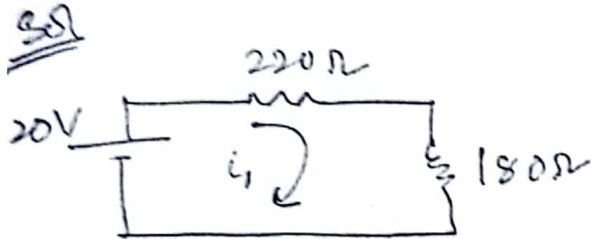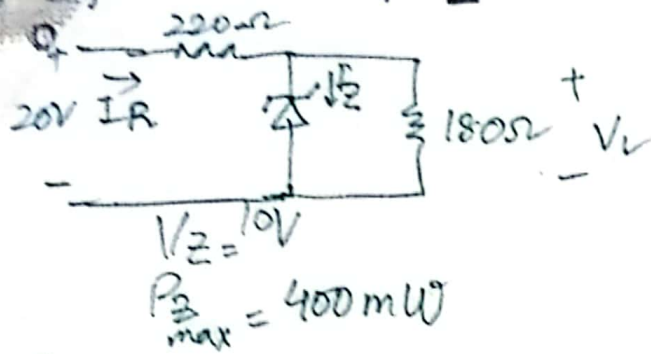find V_L , I_L , I_Z and I_R when $R_L = 180 \text{ ohms}$




apply KVL

$$-20 + 220i + 180i = 0$$

$$i = 0.05A = 50mA$$

$$V_L = IR = 50 \times 10^{-3} \times 180 = 9V$$

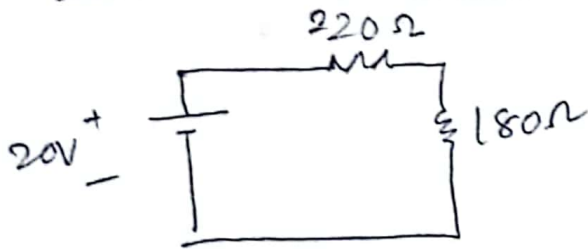Since $9V < 10V$
 the diode will remain ~~off~~




$$V_L = 9V$$

$$I_L = 50mA$$

$$I_Z = 0A$$

$$I_R = 50mA$$

b) repeat for $R_L = 470\Omega$

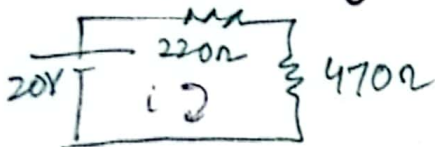

KVL

$$-20 + 220i + 470i = 0$$

$$i = 0.02899A = 28.99mA$$

$$V_L = IR = 28.99 \times 10^{-3} \times 470$$

$$V_L = 13.6V$$

Since $13.6 > 10V$ so
 the diode will turn on



$$V_L = 10V$$

$$I_L = \frac{V}{R} = \frac{10}{470} = 0.0213 = \underline{21.28 \text{ mA}}$$

$$I_Z = \frac{P}{V} = \frac{400 \times 10^{-3}}{10} = \underline{40 \text{ mA}}$$

$$I_R = \frac{V_s - 10}{220} = \frac{20 - 10}{220} = \underline{45.45 \text{ mA}}$$

c) $R_L = ?$ for maximum power of Zener diode

find I_L

$$P = 1W$$

$$I_Z = \frac{400 \times 10^{-3}}{10} = 40 \text{ mA}$$

$$I_{L\min} = I_R - I_Z = (45.45 - 40) \text{ mA} = 5.45 \text{ mA}$$

$$R_L = \frac{V}{I} \text{ (ohm's law)} = \frac{10}{5.45 \times 10^{-3}} = \boxed{1834.9 \Omega}$$

the larger the R_L the lower the I_L , hence greater power

d) minimum value of R_L to turn Z_D on.



applying the voltage divider

$$V_L = 10 = \frac{R_L (20)}{R_L + 220}$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200$$

$$\boxed{R_L = 220 \Omega}$$

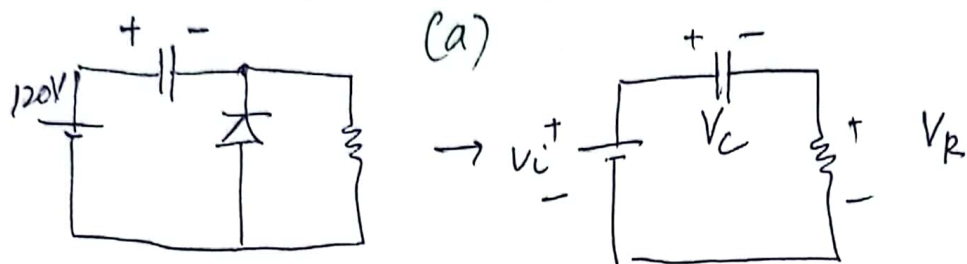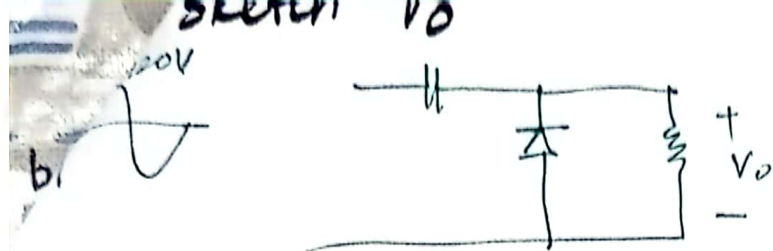

$$\begin{aligned} -V_i + V_c + V_R &= 0 \\ V_c &= 120 - V_R \end{aligned} \quad \left. \vphantom{\begin{aligned} -V_i + V_c + V_R &= 0 \\ V_c &= 120 - V_R \end{aligned}} \right\} \text{+ve cycle}$$


-ve cycle

$$\begin{aligned} +V_i + V_R - V_c &= 0 \\ V_R &= -V_i + V_c \\ &= -120 + 120 - V_R \end{aligned}$$

$$V_R = +240 - V_R$$



$$2V_R = +240$$


$$\boxed{V_R = +120}$$

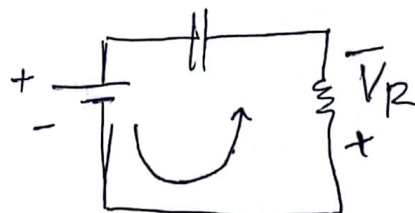

$$V_o = 120 - V_R = 120 - 120 = 0 \text{ V}$$
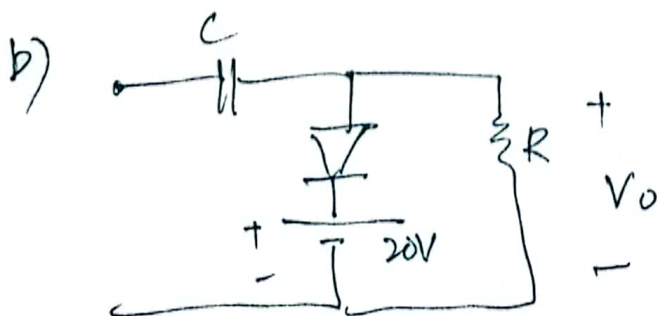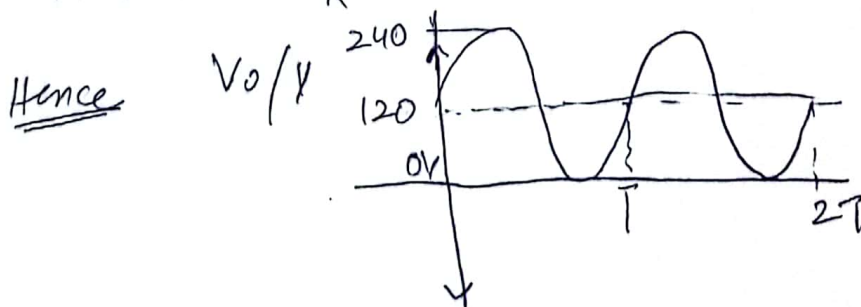
$$\begin{aligned} V_{dc} &= \frac{240 + 0}{2} \\ &= +120 \end{aligned}$$



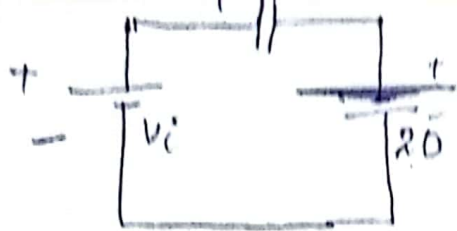

+ve cycle
diode is on

eq KVL

$$-V_i + V_c + 20 = 0$$


$$V_c = V_i - 20$$

$$V_c = 120 - 20 = 100V$$

$$\boxed{V_o = 20V}$$

for -ve cycle

diode is off

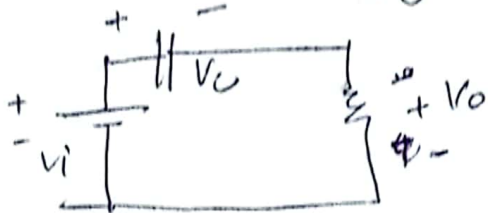


KVL

$$V_i - V_o - V_c = 0$$

$$-V_o = V_c - V_i$$

$$V_o = -100 - 120 = -220$$

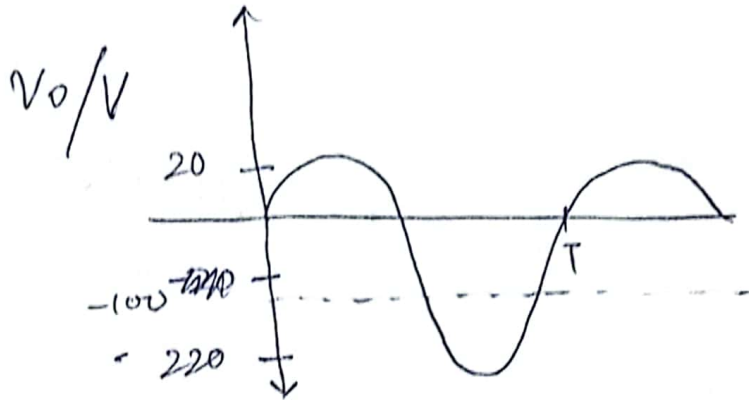

$$V_{dc} = \frac{-220 + 20}{2} = -100$$

The end.